

Class 2

1

Radio Transmitter and Receivers

January 2026


Radio Circuits

2

- From the 1910s to mid 1990s, all radio systems used the same design techniques
- First, everything was done with vacuum tubes
- Then, transistors
- Then, integrated Circuits
- Later, Large Scale Integrated Circuits (complete designs on one IC)
- Then, in the 1990s, computers became fast enough that designs started to be developed in software
- Now almost all radio systems are implemented in Software and called Software Designed Radios (SDRs)
- For this class we will discuss the designs of the 20th century
- We will not be discussing SDRs


January 2026

Continuous Wave (CW) Transmitter

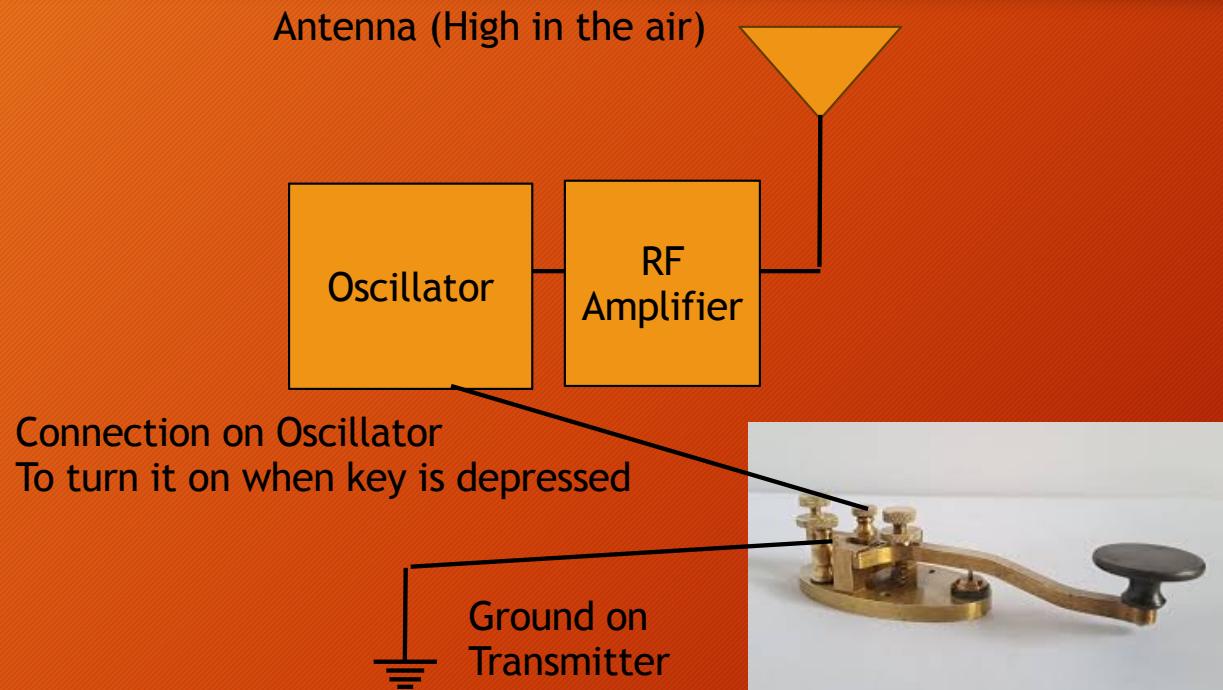


January 2026

Amplitude Modulation (AM) Transmitter

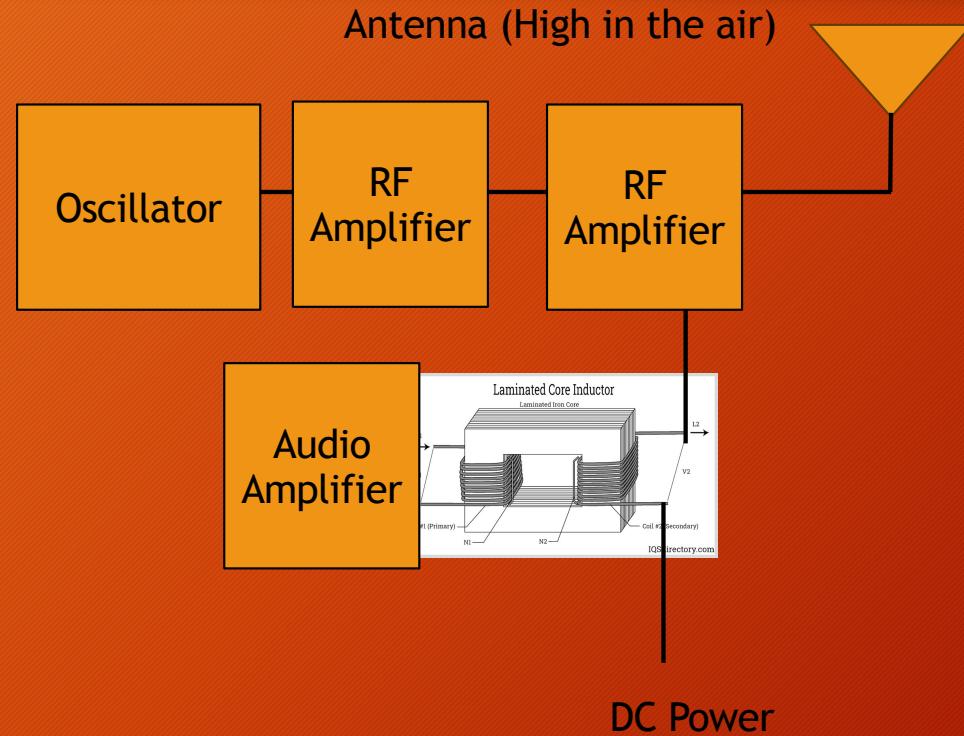

500 Watt Vacuum Tube AM Transmitter

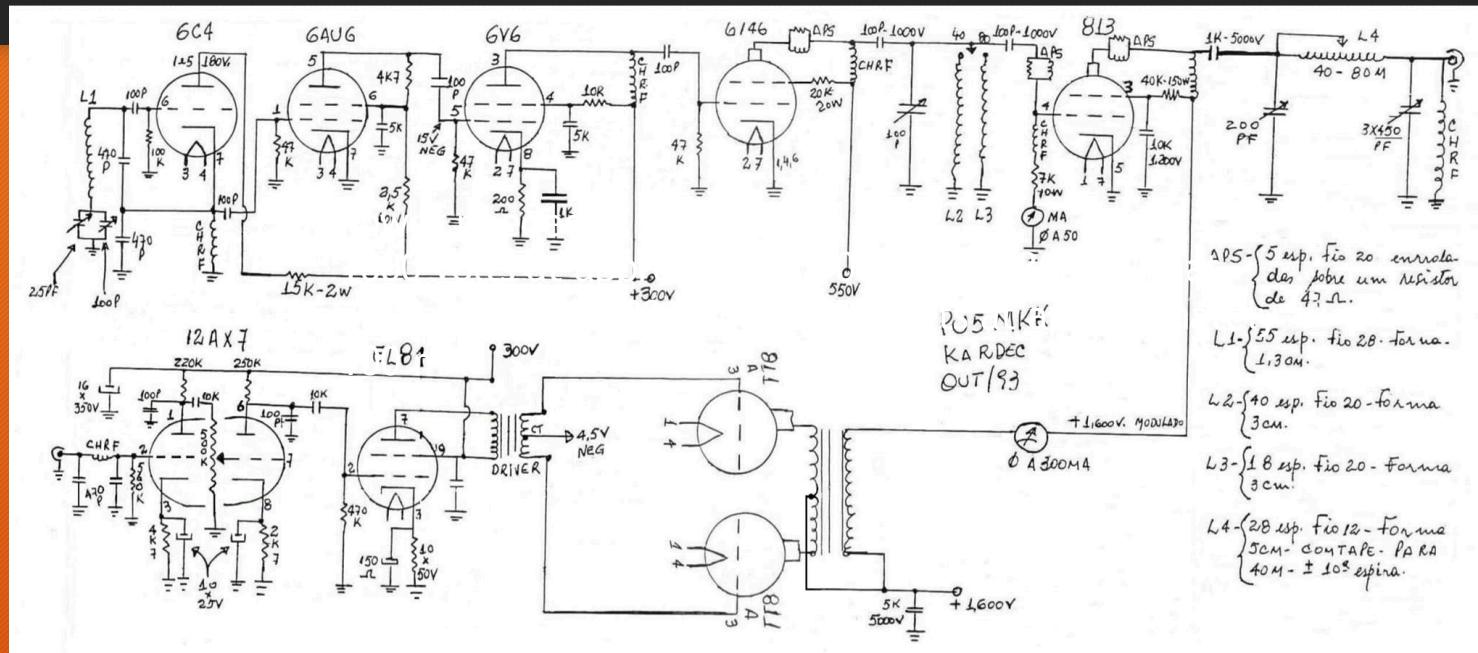


Power needed:

1600 volts at approximately 0.5 Amps, 300 volts at approximately 100 mA and
550 volts at approximately 100 mA

Single Side Band Transmitter (SSB) - Filter


6

January 2026

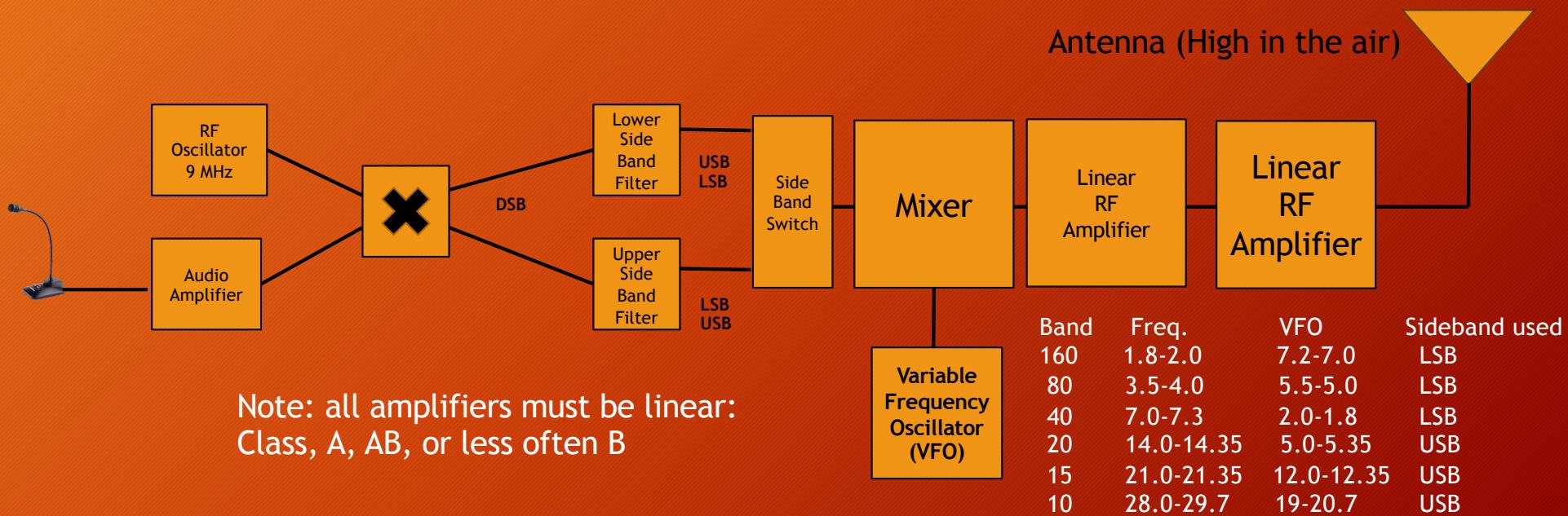


Single Side Band Transmitter (SSB) - Phasing

January 2026

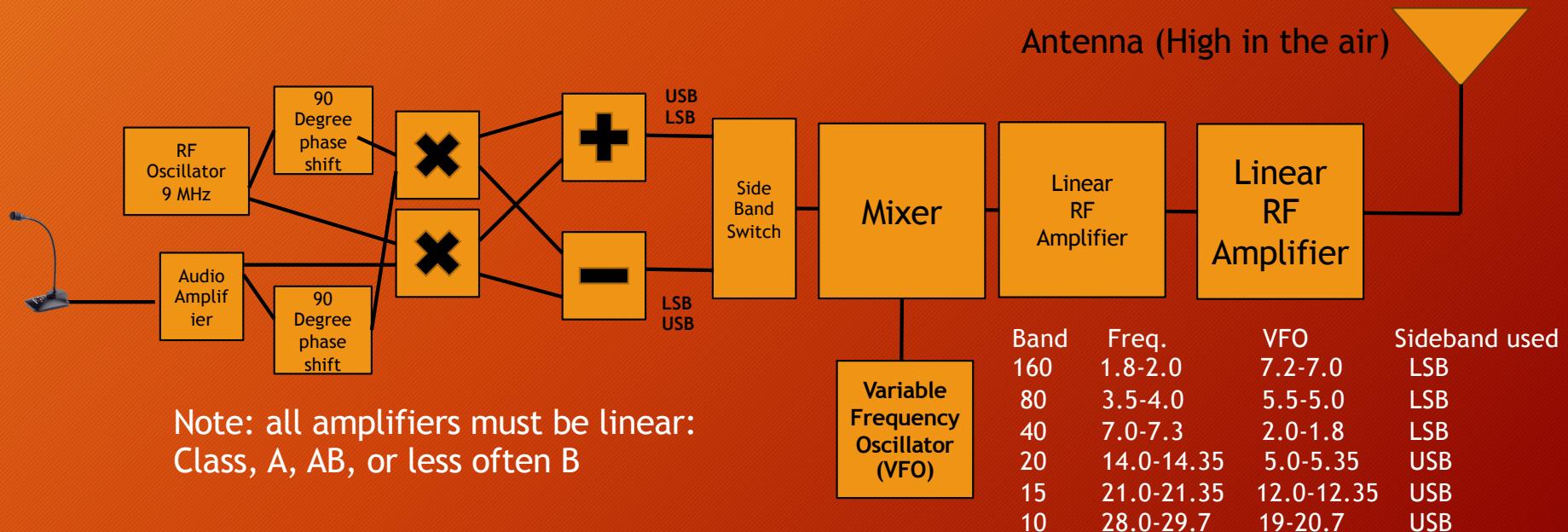


How the VFO is constructed

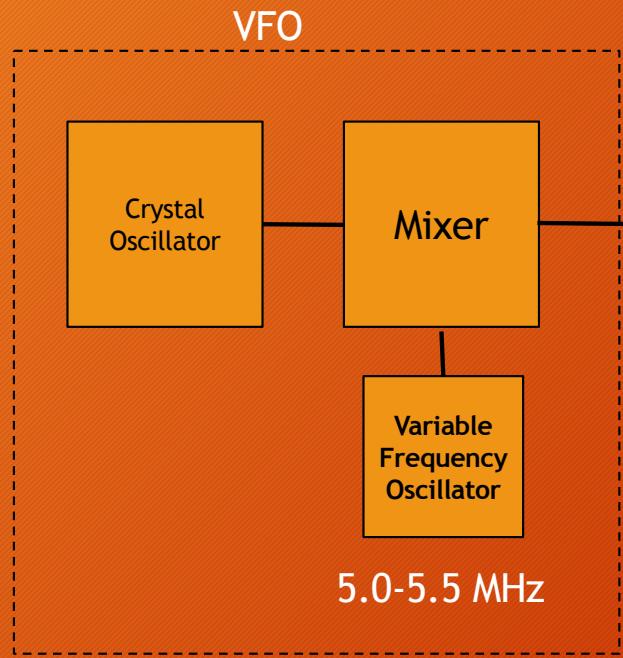

| Band | Freq. | Internal Oscillator | Crystal | VFO | Sideband used |
|------|------------|---------------------|---------|------------|---------------|
| 160 | 1.8-2.0 | 5.5-5.3 | 1.7 | 7.2-7.0 | LSB |
| 80 | 3.5-4.0 | 5.5-5.0 | none | 5.5-5.0 | LSB |
| 40 | 7.0-7.3 | 5.5-5.3 | 3.5 | 2.0-1.8 | LSB |
| 20 | 14.0-14.35 | 5.0-5.35 | none | 5.0-5.35 | USB |
| 15 | 21.0-21.35 | 5.0-5.35 | 7.0 | 12.0-12.35 | USB |
| 10 | 28.0-29.5 | 5.0-5.5 | 14.0 | 19.0-19.5 | USB |
| 10 | 28.5-29.0 | 5.0-5.5 | 14.5 | 19.5-20.0 | USB |
| 10 | 29.0-29.5 | 5.0-5.5 | 15.0 | 20.0-20.5 | USB |
| 10 | 29.5-29.7 | 5.0-5.2 | 15.5 | 20.5-20.7 | USB |


Modern Radio Block Diagram

January 2026

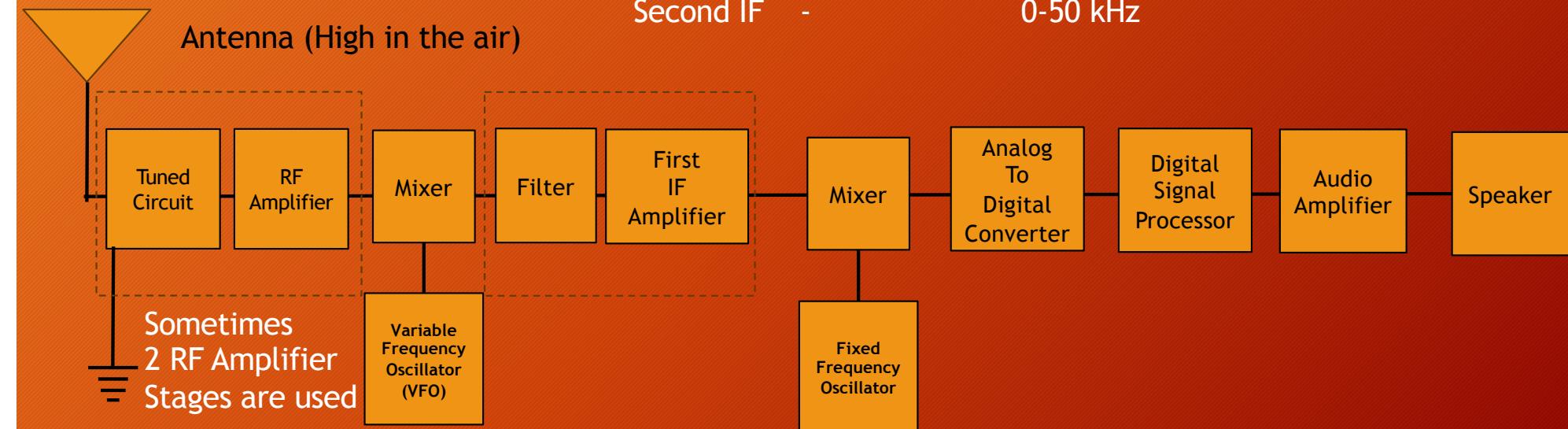

Flex Radio 6600 Block Diagram


10

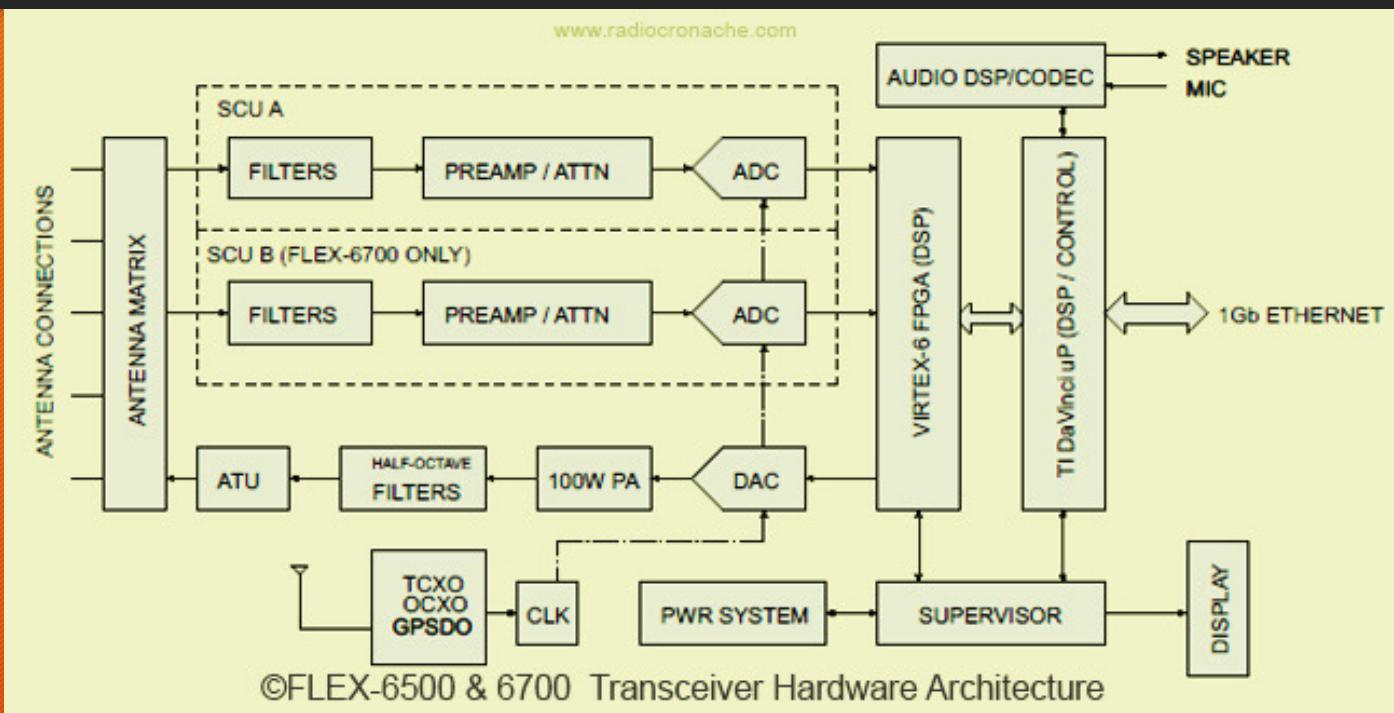

January 2026

Frequency Modulation (FM) transmitter Pre 1980s

11

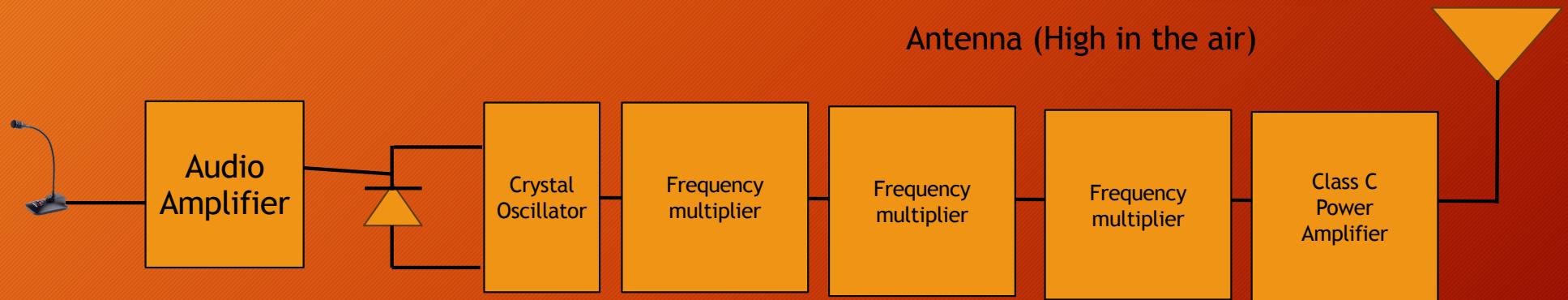

For 2 meters:

| | | | |
|--------------|----|-------------|-------------|
| 8.169166 MHz | x3 | x3 | x2 |
| 24.5075 MHz | | 73.5225 MHz | 147.045 MHz |

For 6 meters:

| | | | |
|------------|----|----------|-----------|
| 8.6033 MHz | x3 | x3 | x2 |
| 25.81 MHz | | not used | 51.62 MHz |

January 2026

Modern FM Transmitters

12

- Designs since the mid 1980s have eliminated the use of frequency specific crystals and
- Channel Crystals replaced by frequency synthesizers that use a computer to generate all need frequencies

January 2026


Tuned Radio Frequency (TRF) Receiver

13

- In a TRF receiver, there are multiple stages of amplification at the radio frequency of the transmitter
- The more stages of amplification, the more sensitive the receiver
- Unfortunately, multiple stages often have stray inductance and capacitance the results in the output of the receiver being fed back into the input resulting in oscillations


TRF Block Diagram

14

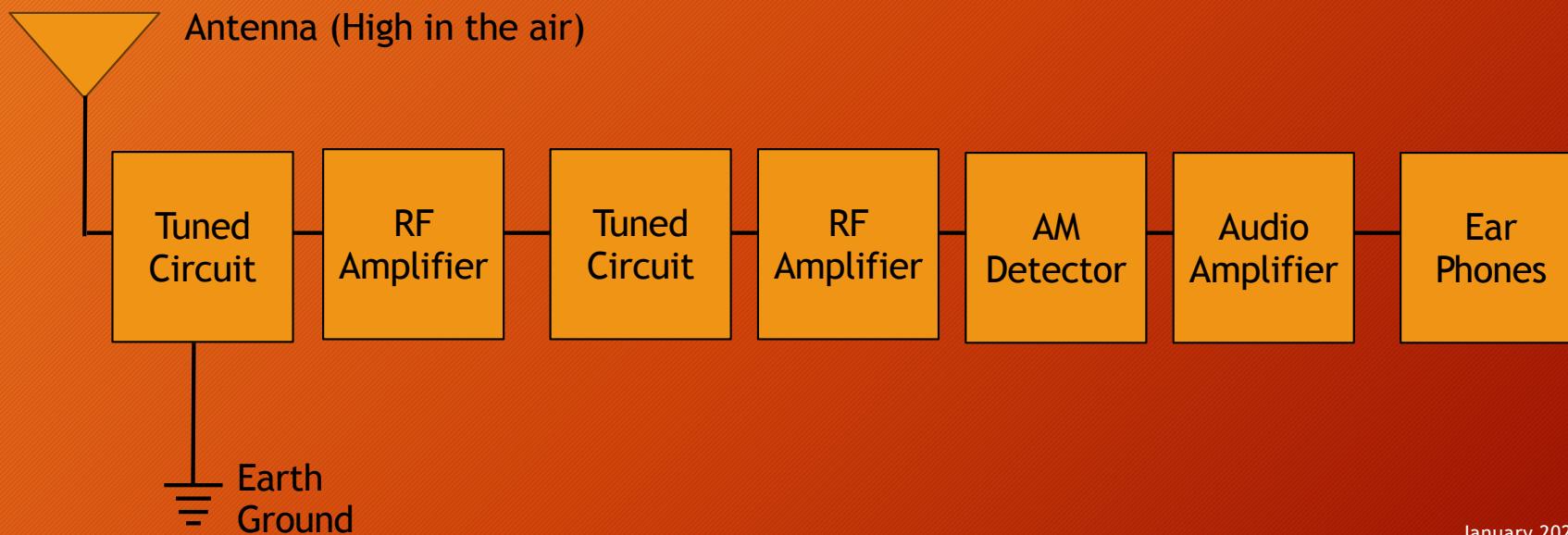

January 2026

Example: Simple TRF Receiver

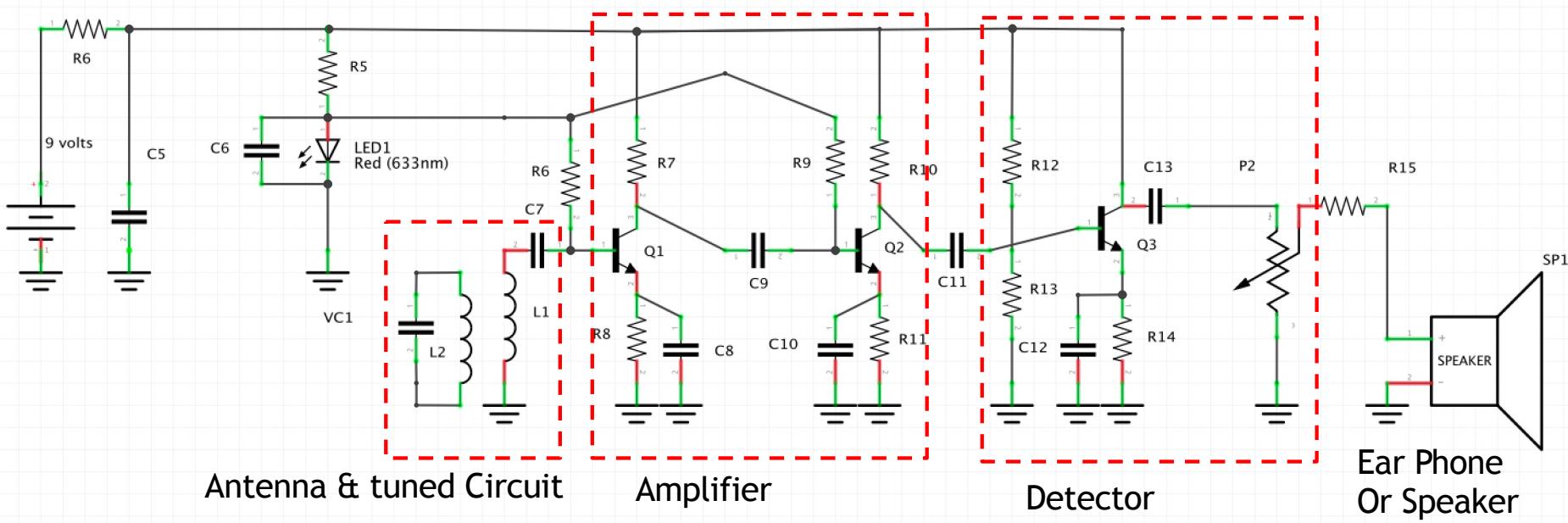

Regenerative Receiver


16

- The original patent for the regenerative receiver was filed by Edwin Armstrong in 1914
- He demonstrated it at the Marconi site (across the road from CDL)
- It uses an RF amplifier that feeds some of the output back into the input
- The amount of feedback is adjusted by a regeneration control and is adjust to make the amplifier gain be just before it starts oscillating
- A regenerative receiver can be made very sensitive to receiver very weak signals
- The regeneration stage typically also detects the AM signal
- Putting it into oscillation can make it receiver CW signals

January 2026


Block Diagram of Regenerative Receiver

17

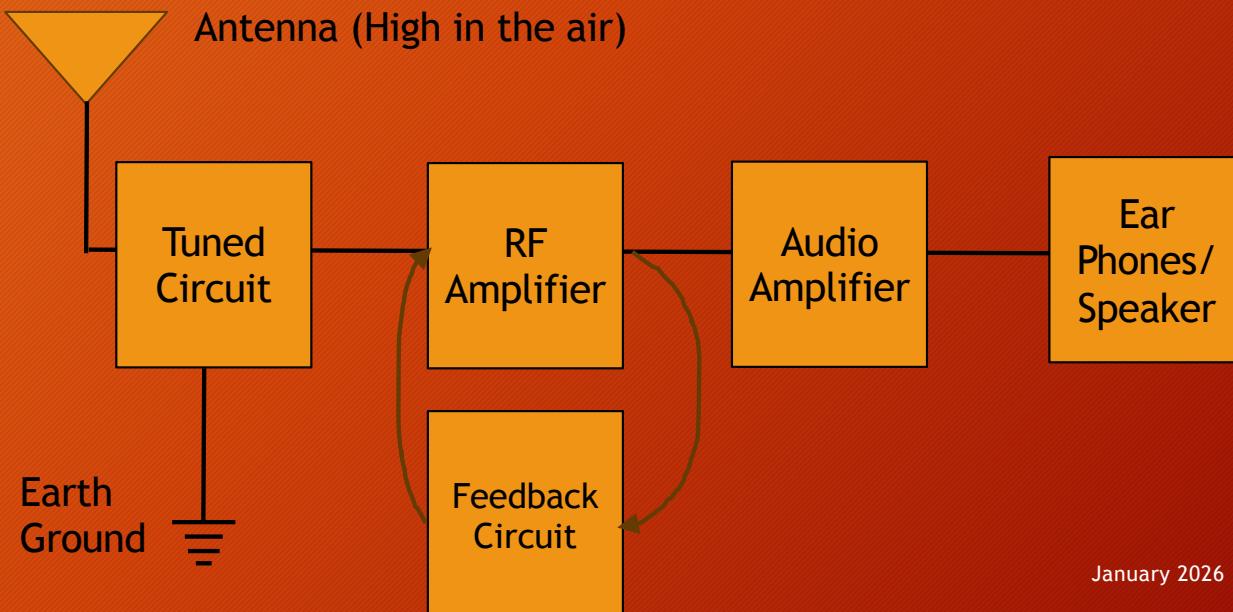


January 2026

Example Regenerative Receiver with Tubes

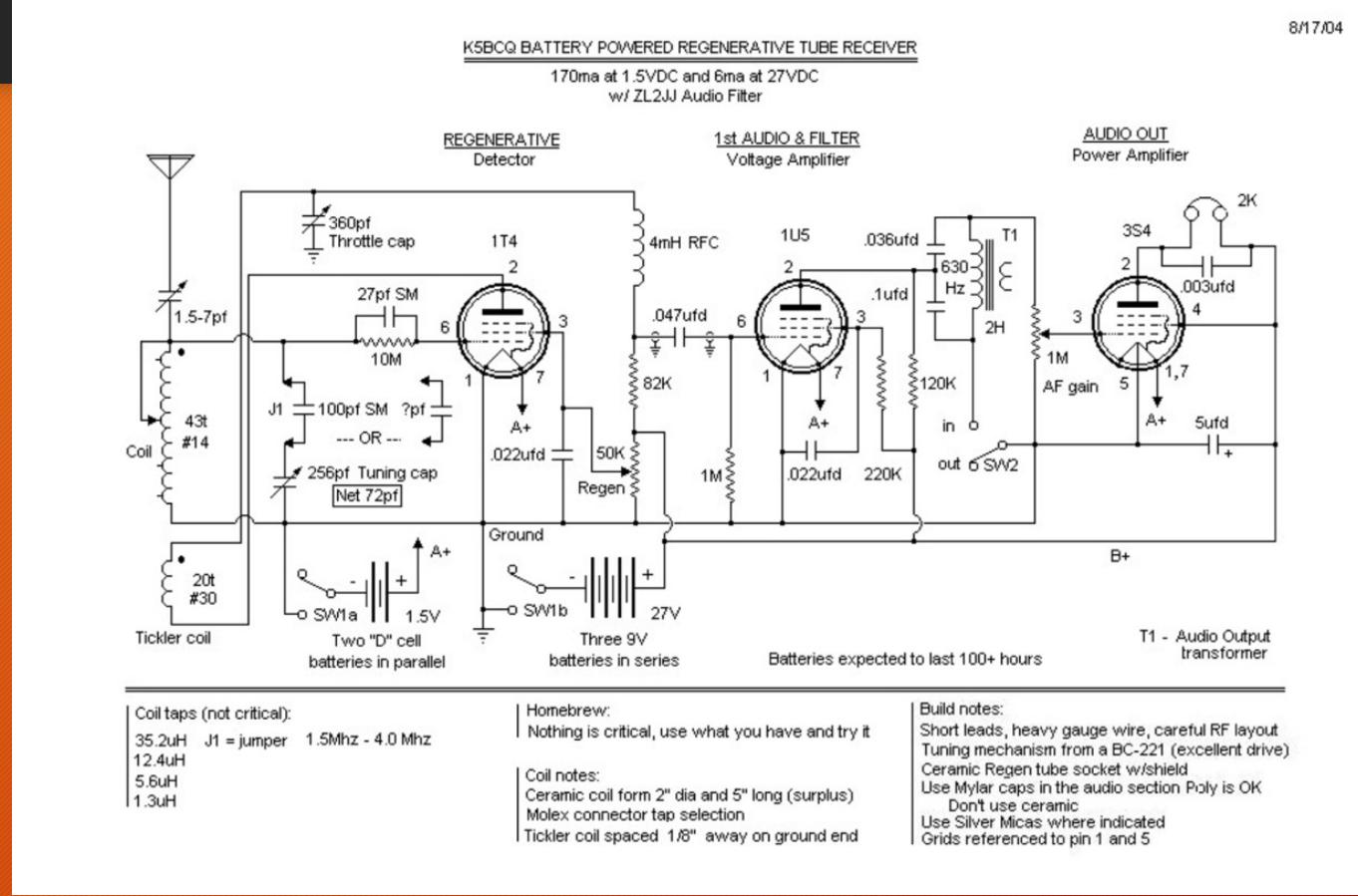

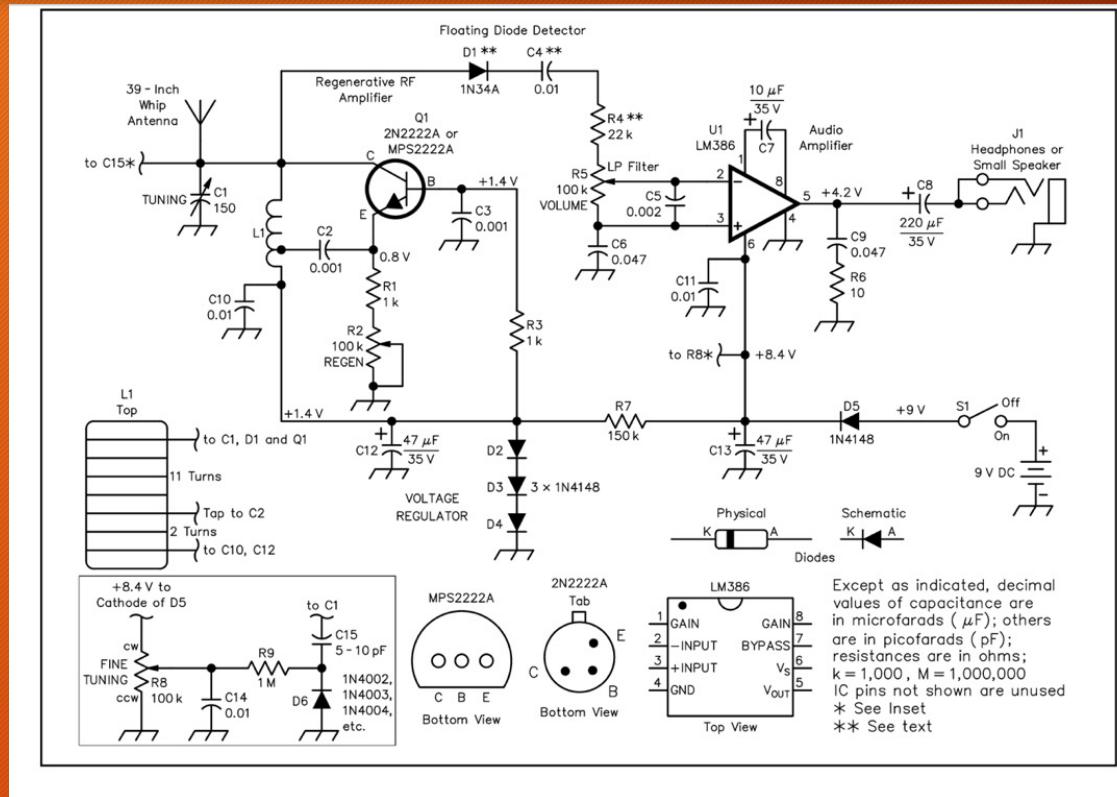Example Regenerative Receiver with Transistors and Integrated circuits



Simple Regen Receiver From QST


January 2026

Super-Regenerative Receiver

20

- In a Super Regenerative Receiver, the circuit is made to in and out of oscillation at a rate around 50,000-100,000 times per second
- Thus no regeneration control is needed
- The receiver is very sensitive

Example Super- Regenerative Receiver

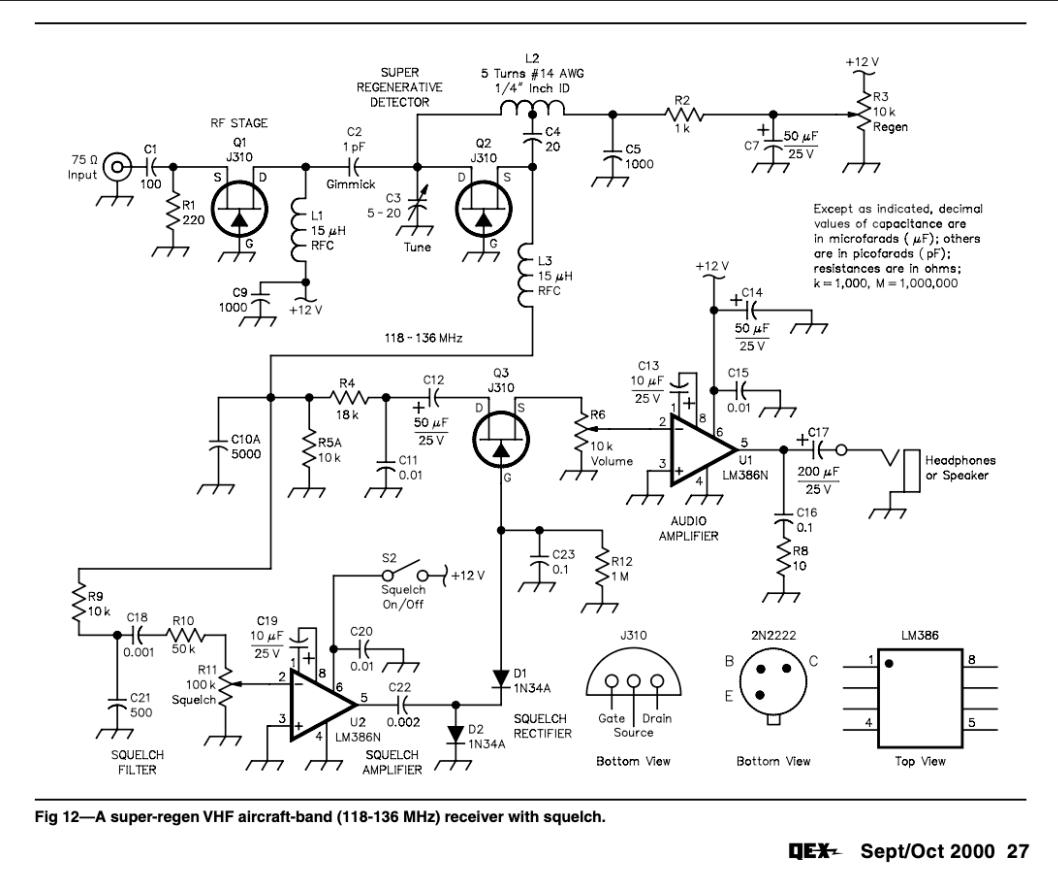

QEX Sept/Oct 2000 27

Can be found on arrl.org
[new_super_regen_for_vhf_uhf_2000_09qex018.pdf](http://arrl.org/new_super_regen_for_vhf_uhf_2000_09qex018.pdf)

January 2026

Disadvantages of Regenerative Receiver

22

- It takes skill to adjust the receiver
- The control needs to be adjusted often from:
 - The antenna swaying in the wind
 - Changes in frequency of the receiver
- When a super regenerative or regenerative receiver goes into oscillation it radiates a signal like a transmitter
 - This can interfere with other receivers nearby
 - The Nazi's used this to direction find underground stations when the operators mis-adjusted their receivers and left them on

January 2026


Superheterodyne Receiver

23

- Lucien Lévy: Patented the fundamental circuit scheme for the superheterodyne receiver in 1917
- Edwin H. Armstrong: Developed a more practical version of the superheterodyne method and was granted U.S. patent 1,342,885 in 1920 for his work
- In a Superheterodyne receiver, the received frequency is changed to a (typically) lower frequency where
 - Gain and
 - Selectivity is easier to design into the circuits

January 2026

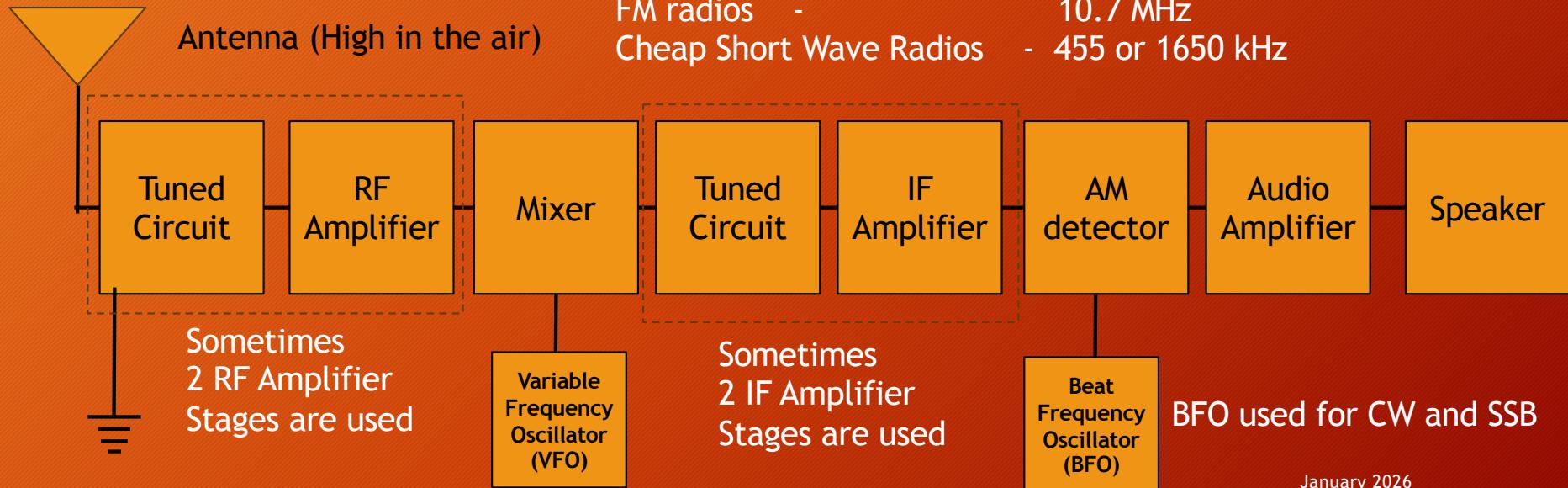
Block Diagram of Superheterodyne Receiver




Block Diagram of Double Conversion Superheterodyne Receiver

25

January 2026

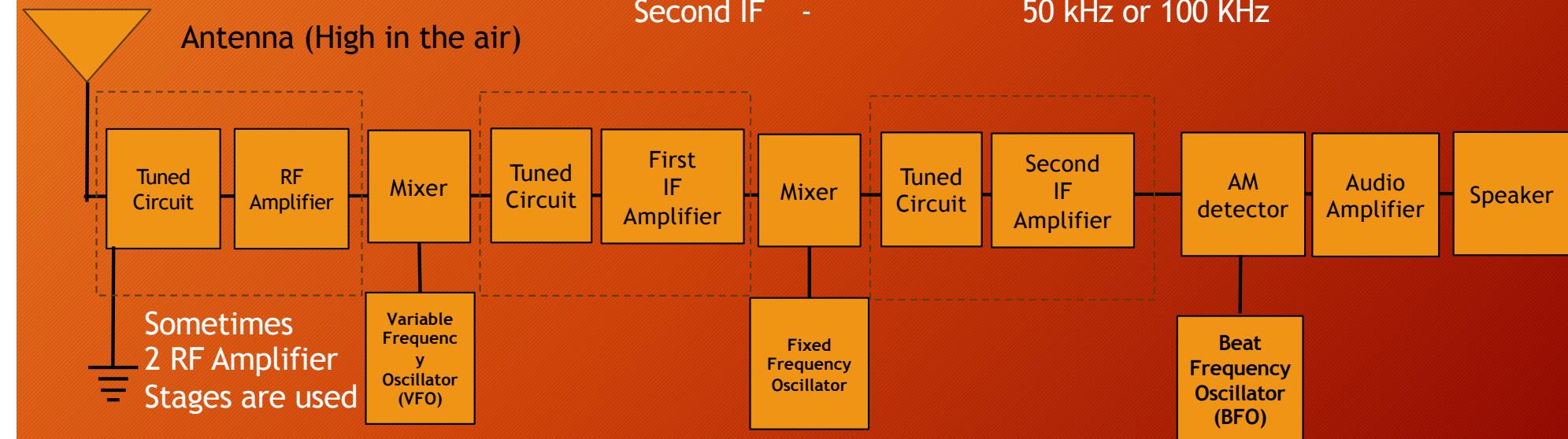

Superhet Receiver from RCA Tube Manual

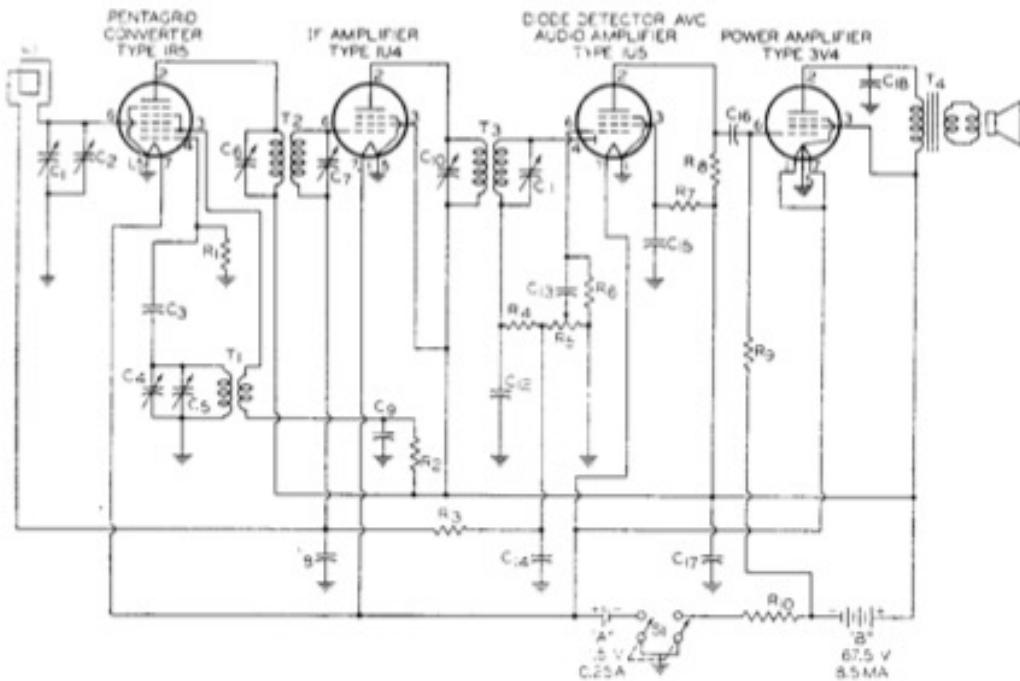


C₁, C₄ = Ganged tuning capacitors; C₁, 10-274 μf ; C₄, 7.5-122.5 μf
 C₂, C₅ = Trimmer capacitors, 2-15 μf
 C₃ = 56 μf , ceramic
 C₆, C₇, C₁₀, C₁₁ = Trimmer capacitors for if transformers
 C₈ = 0.05 μf , paper, 50 v.
 C₉, C₁₂ = 0.02 μf , paper, 100 v.
 C₁₃ = 82 μf , ceramic
 C₁₄, C₁₅ = 0.002 μf , paper, 150 v.
 C₁₆ = 33 μf , ceramic

C₁₈ = 10 μf , electrolytic, 100 v.
 C₁₉ = 0.0022 μf , paper, 600 v.
 L₁ = Loop antenna, 540-1600 Ke
 R₁ = 100000 ohms, 0.25 watt
 R₂ = 15000 ohms, 0.25 watt
 R₃ = 3.3 megohms, 0.25 watt
 R₄ = 68000 ohms, 0.25 watt
 R₅ = Volume control, potentiometer, 2 megohms
 R₆ = 10 megohms, 0.25 watt
 R₇ = 4.7 megohms, 0.25 watt
 R₈, R₉ = 1 megohm, 0.25 watt
 R₁₀ = 390 ohms, 0.25 watt
 S₁ = Switch, double-pole, single-throw
 T₁ = Oscillator coil for use with tuning capacitor of 7.5-122.5 μf , and 455 Ke if transformer
 T₂, T₃ = Intermediate-frequency transformers, 455 Ke
 T₄ = Output transformer for matching impedance of voice coil to 10000-ohm tube load

Demodulation of AM

27

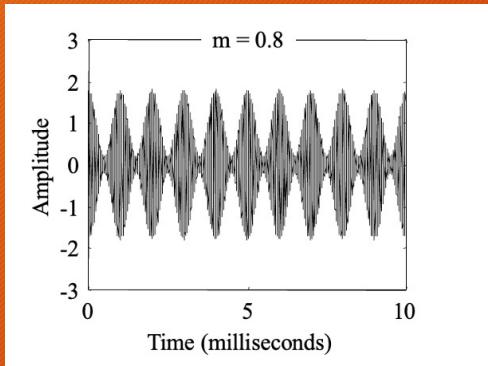
- The simplest way to detect AM is to rectify the received signal
- Then filter out the RF leaving just the audio signal



Diode
Rectifier



RF Filter

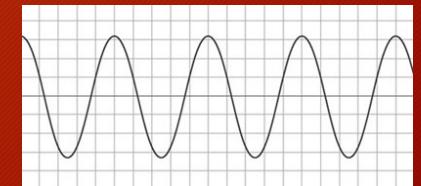


January 2026

Demodulation of CW

28

- The simplest way to demodulate CW is to use an AM detector and add an RF or IF signal 400 Hz to 1.5 Hz from the received signal
- The detector mixes the two signals together and generates a tone when the CW signal is present

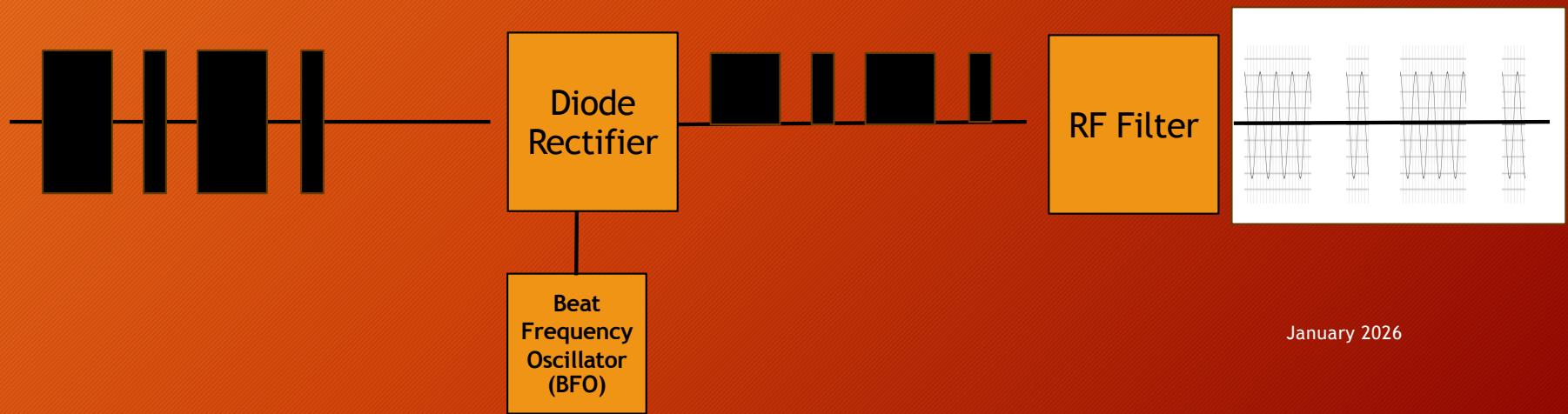

January 2026

Demodulation of Single Side Band (SSB)


29

- Demodulation of SSB is similar to that of CW
- But the BFO signal needs to be within less than 100 Hz of the missing carrier signal
- Early SSB receivers tended to drift off frequency and the received signal had distortion that made it sound like “Donald Duck”
- This limited adoption of SSB in the 50s and 60s
- Modern SSB receivers use a mixer instead of an AM detector
- They also can be tuned and stay tuned to within a few Hz of the mixing carrier
- The speech sounds natural

January 2026


Demodulation of FM and PM

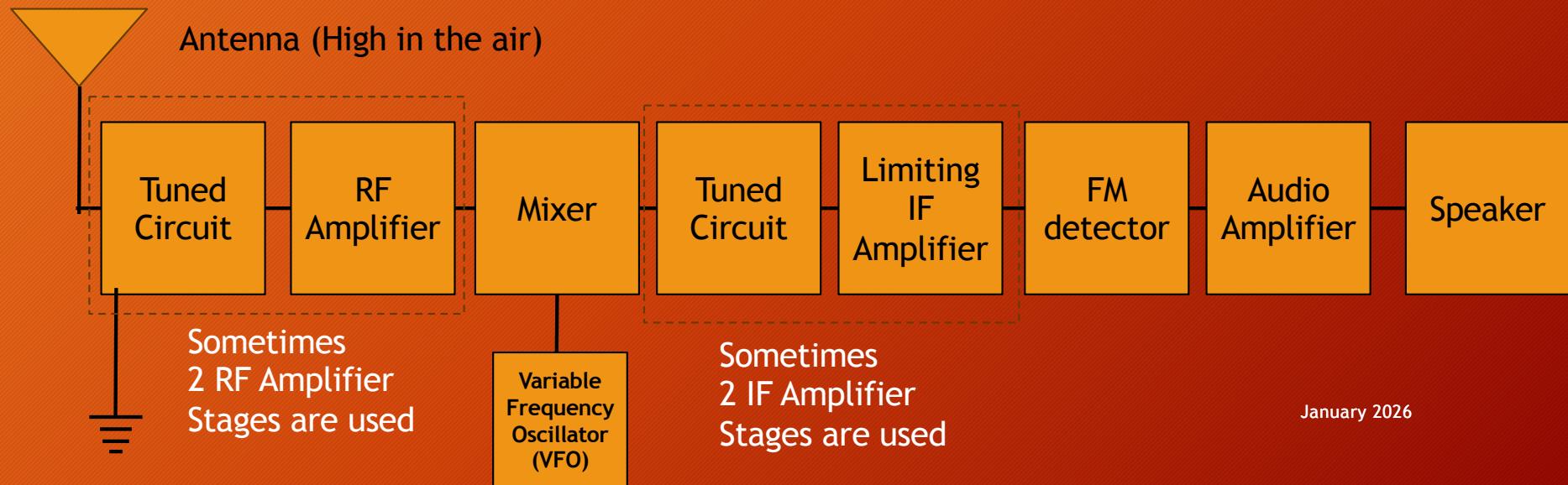- Demodulation of FM in a receiver needs to additional circuits compared to an AM receiver
- An IF amplifier that limits the maximum signal and thus clips it to a constant level
- An FM detector that uses a special coil called a discriminator coil and two diodes



Discriminator Operation

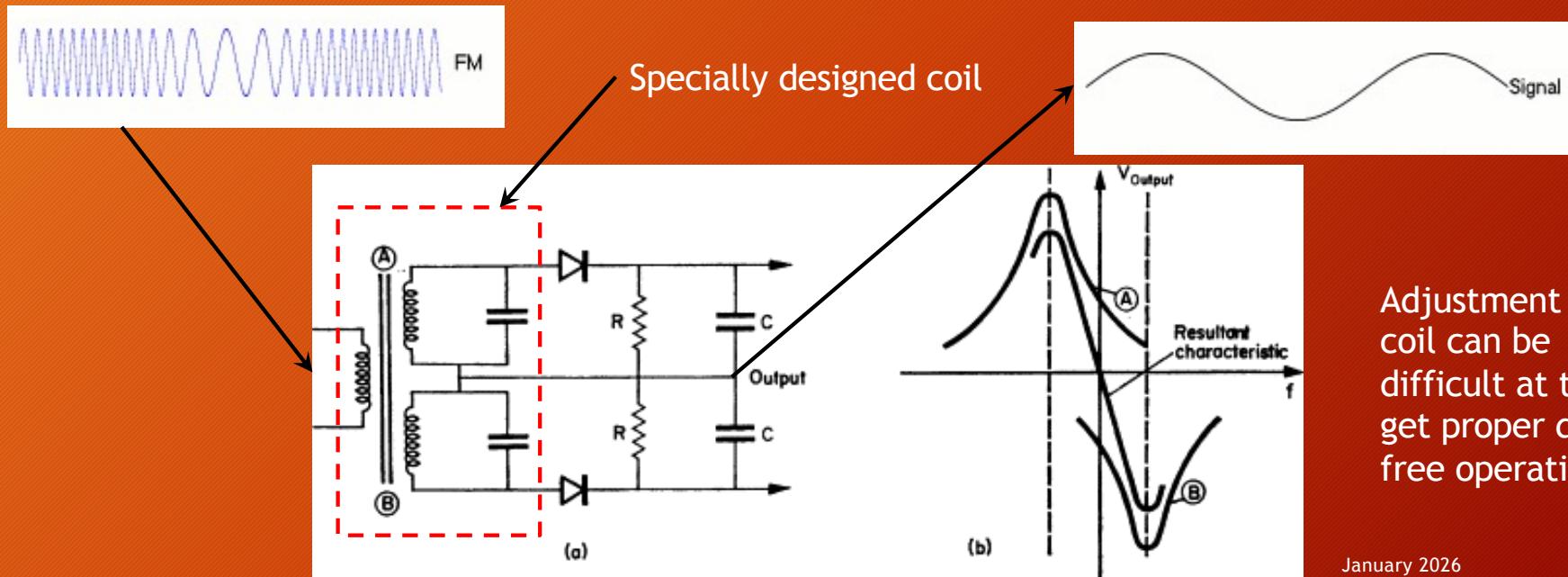The output changes with the changes in frequency



Adjustment of the coil can be difficult at times to get proper distortion free operation

References

32

- Recommended Textbooks
- ARRL: *The ARRL Handbook for Radio Communications*
- Make: *Radio*
- *Old but still good reference:*
- Rappaport, *Wireless Communications: Principles and Practice*
- Goldsmith, *Wireless Communications*
- Molisch, *Wireless Communications*
- Garg and Wilkes, *Wireless and Personal Communications Systems*
- Useful Online Resources
- FCC Spectrum Allocation Charts
- 3GPP Specifications (for LTE/5G)
- IEEE 802.11 Standards overview
- ITU Radio Regulations
- Simulation Tools
- MATLAB/Simulink Wireless Toolbox
- Python libraries: scipy, matplotlib, commpy
- Free online spectrum analyzers & demos

January 2026