


# Class 2

Analog Radio Transmitter and Receivers


# Radio Circuits

- From the 1910s to mid 1990s, all radio systems used the same design techniques
- First, everything was done with vacuum tubes
- Then, transistors
- Then, integrated Circuits
- Later, Large Scale Integrated Circuits (complete designs on one IC)
- Then, in the 1990s, computers became fast enough that designs started to be developed in software
- Now almost all radio systems are implemented in Software and called Software Designed Radios (SDRs)
- For this class we will discuss the designs of the 20<sup>th</sup> century
- We will not be discussing SDRs


# Continuous Wave (CW) Transmitter

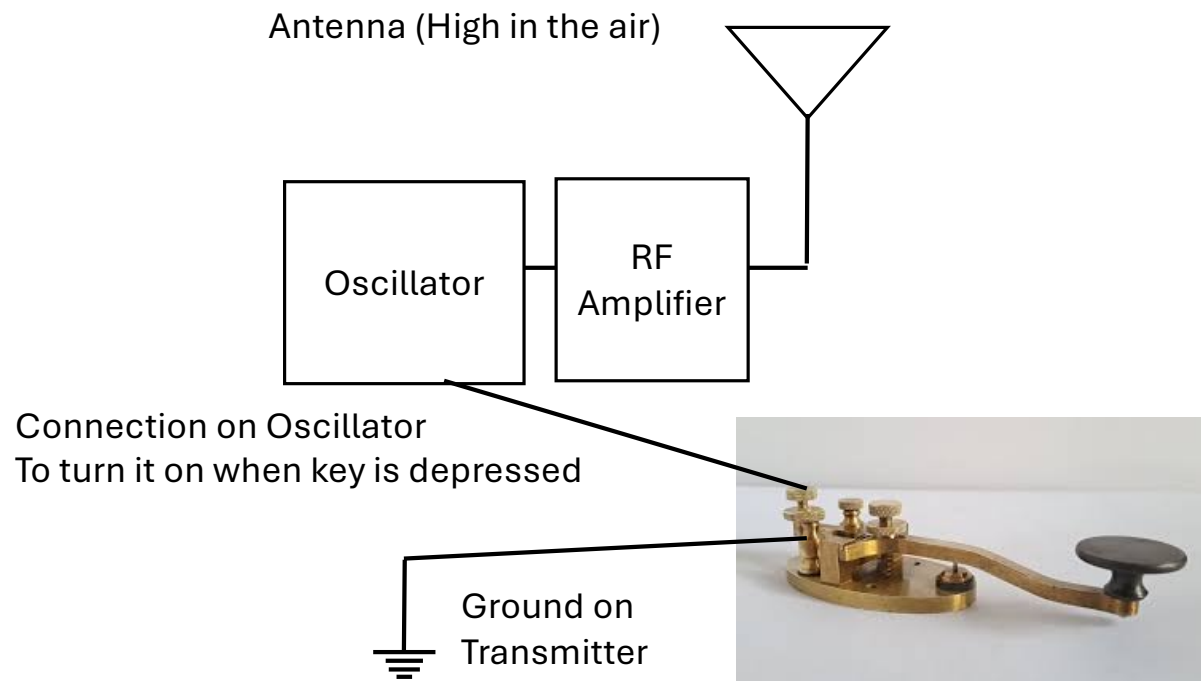

# Amplitude Modulation (AM) Transmitter

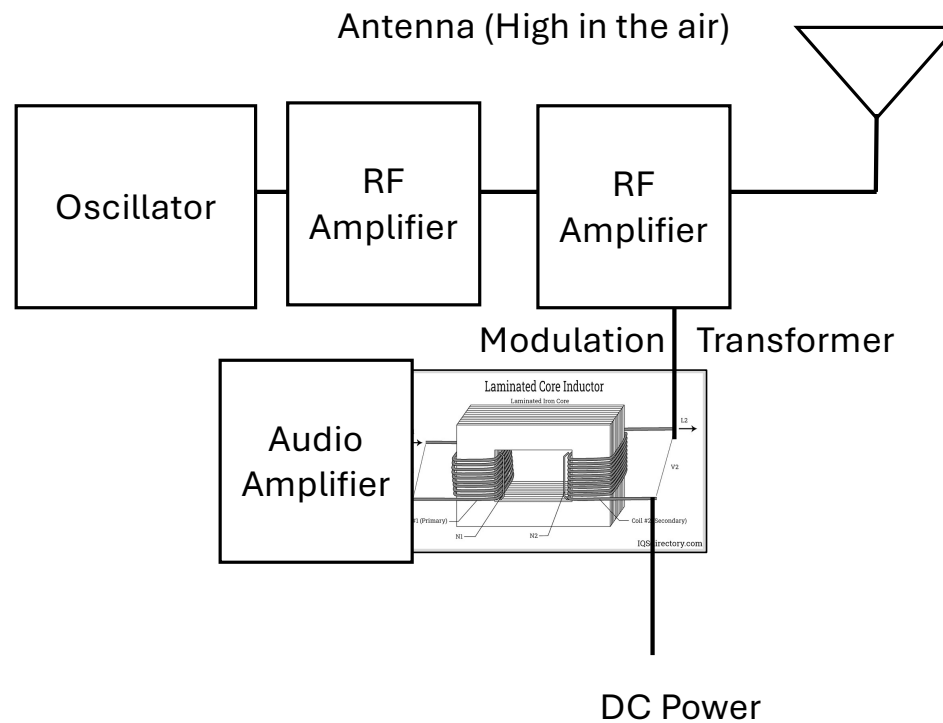


# 500 Watt Vacuum Tube AM Transmitter

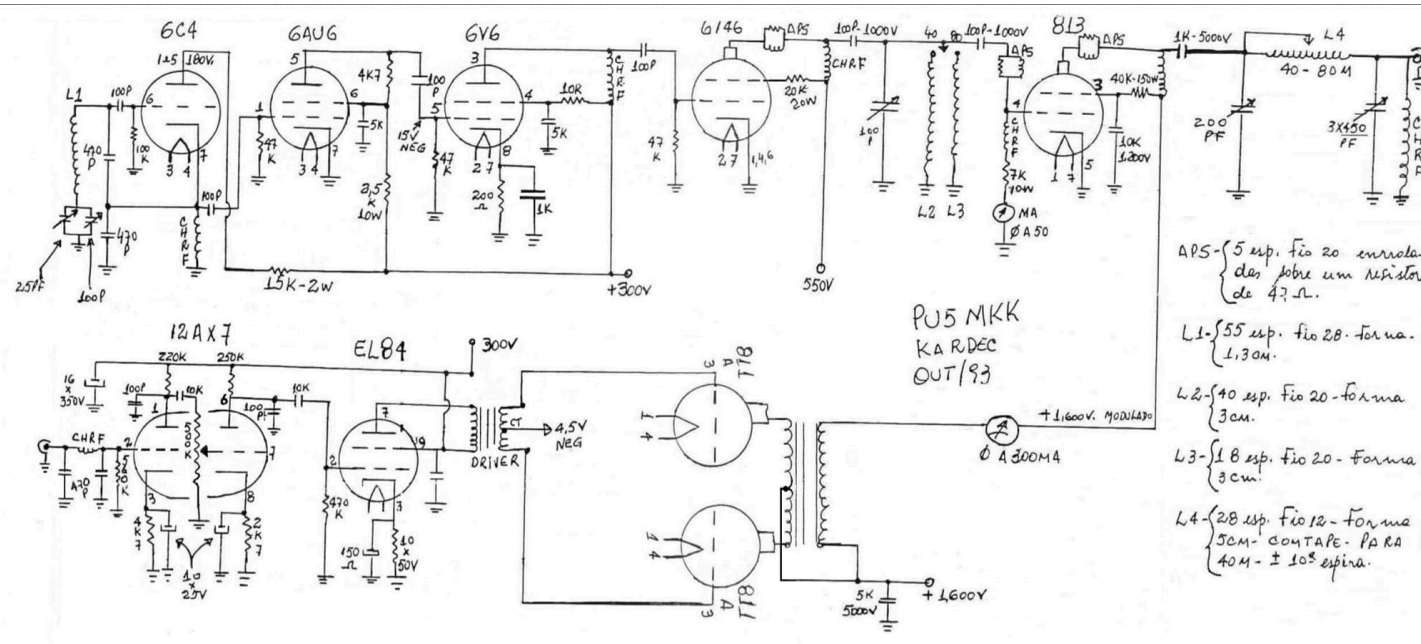


Power needed:

1600 volts DC at approximately 0.5 Amps, 300 volts DC at approximately 100 mA and 550 volts DC at approximately 100 mA,  
10 volts AC 10 amps, 6.3 volts AC at about 10 amps, -4.5 volts at about 0 amps

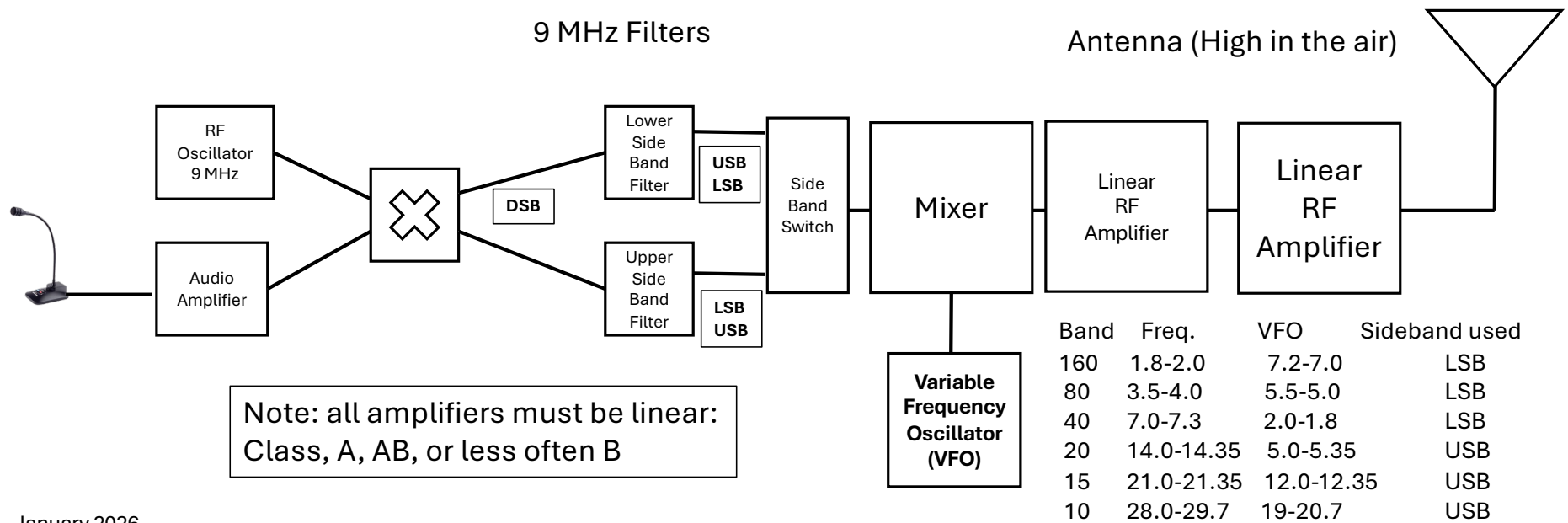
# Single Side Band Transmitter (SSB) - Filter


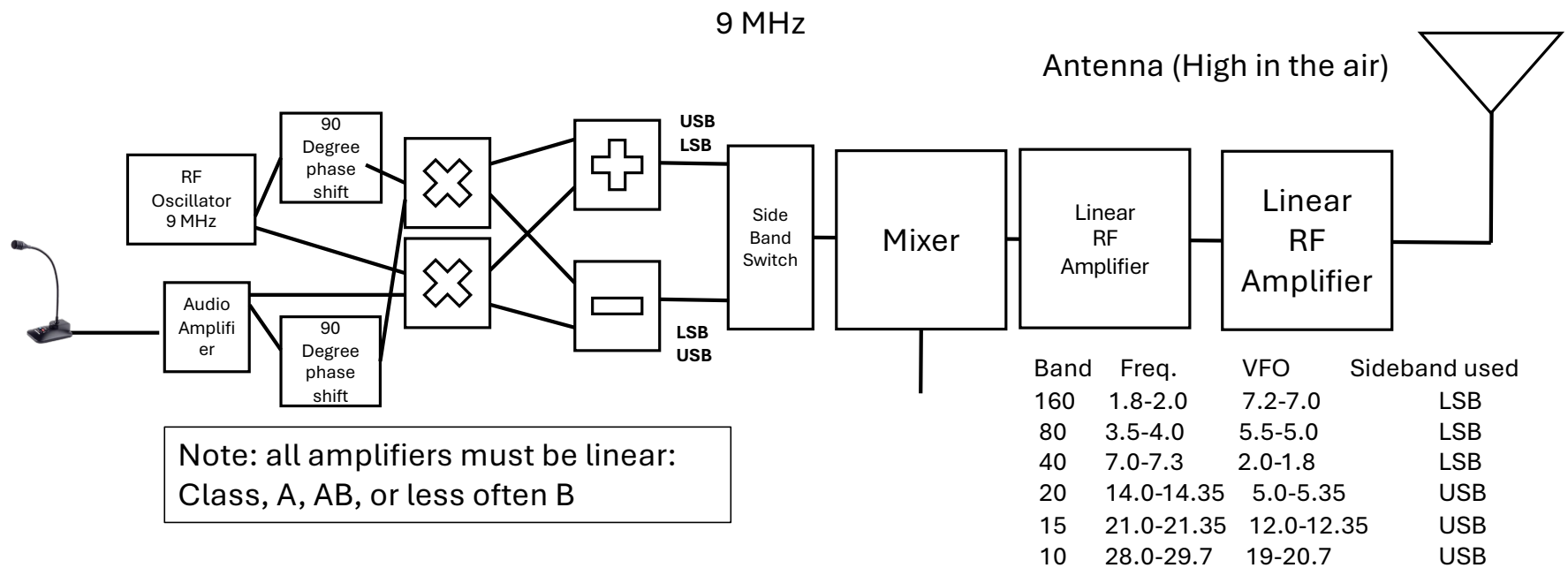
# Single Side Band Transmitter (SSB) - Phasing



# How the VFO is constructed

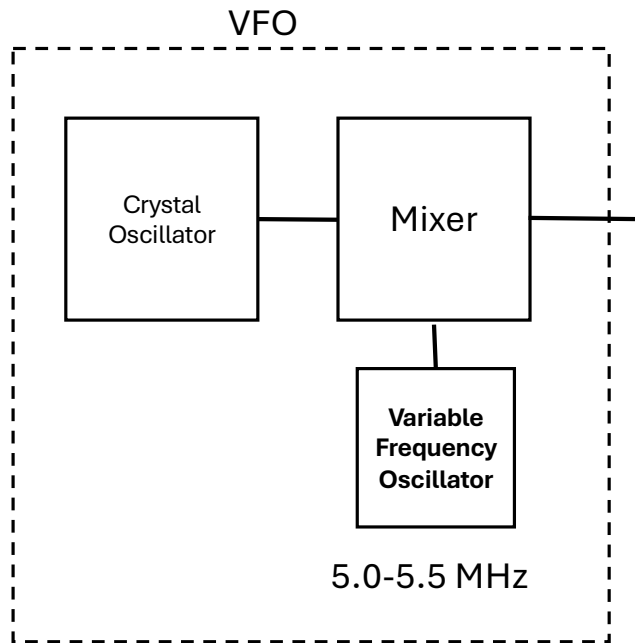


Band	Freq.	Internal Oscillator	Crystal	VFO	Sideband used
160	1.8-2.0	5.5-5.3	1.7	7.2-7.0	LSB
80	3.5-4.0	5.5-5.0	none	5.5-5.0	LSB
40	7.0-7.3	5.5-5.3	3.5	2.0-1.8	LSB
20	14.0-14.35	5.0-5.35	none	5.0-5.35	USB
15	21.0-21.35	5.0-5.35	7.0	12.0-12.35	USB
10	28.0-29.5	5.0-5.5	14.0	19.0-19.5	USB
10	28.5-29.0	5.0-5.5	14.5	19.5-20.0	USB
10	29.0-29.5	5.0-5.5	15.0	20.0-20.5	USB
10	29.5-29.7	5.0-5.2	15.5	20.5-20.7	USB



# Frequency Modulation (FM) transmitter
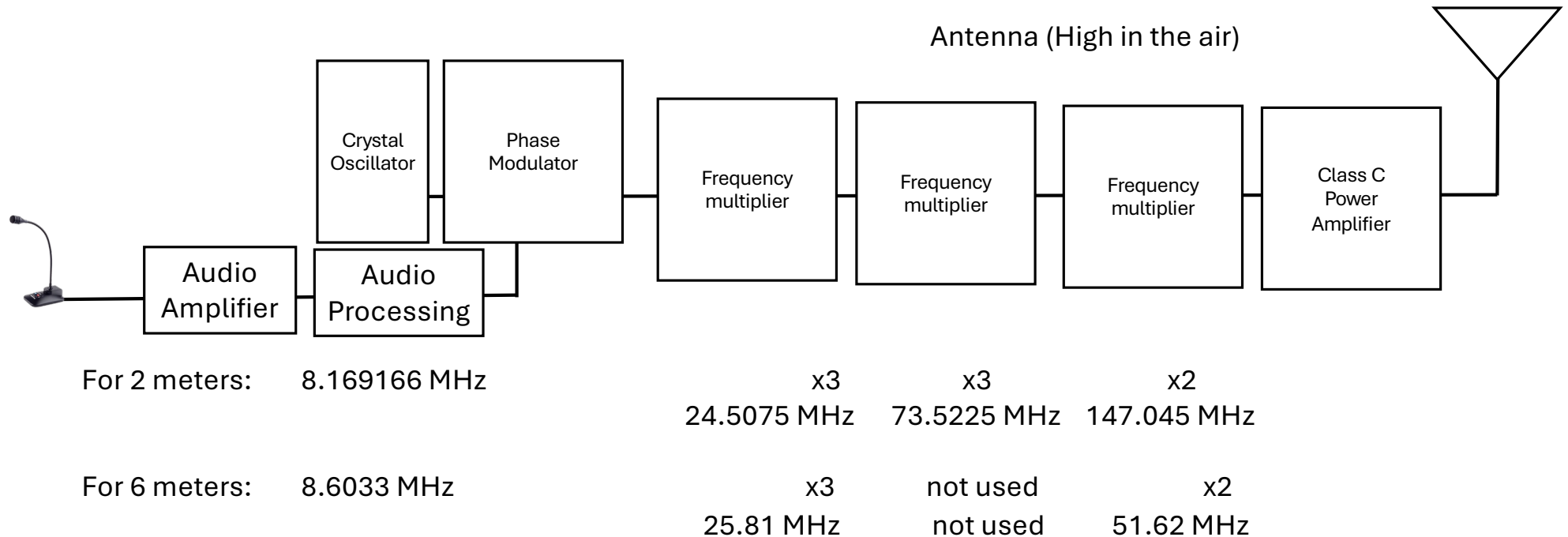
## Pre 1980s

NOTE: FM is created by making an PM transmitter and doing audio processing




# Modern FM Transmitters

- Designs since the mid 1980s have eliminated the use of frequency specific crystals and
- Channel Crystals replaced by frequency synthesizers that use a computer to generate all need frequencies


# Tuned Radio Frequency (TRF) Receiver

- In a TRF receiver, there are multiple stages of amplification at the radio frequency of the transmitter
- The more stages of amplification, the more sensitive the receiver
- Unfortunately, multiple stages often have stray inductance and capacitance that results in the output of the receiver being fed back into the input, thus resulting in oscillations

# TRF Block Diagram

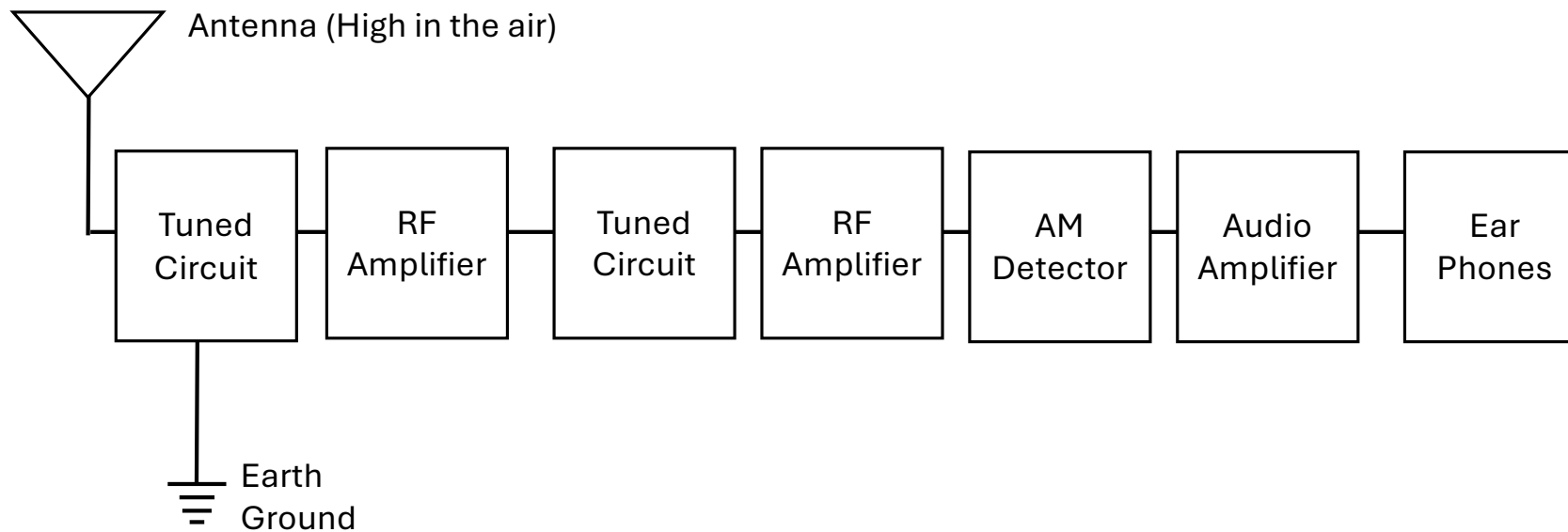


# Example: Simple TRF Receiver

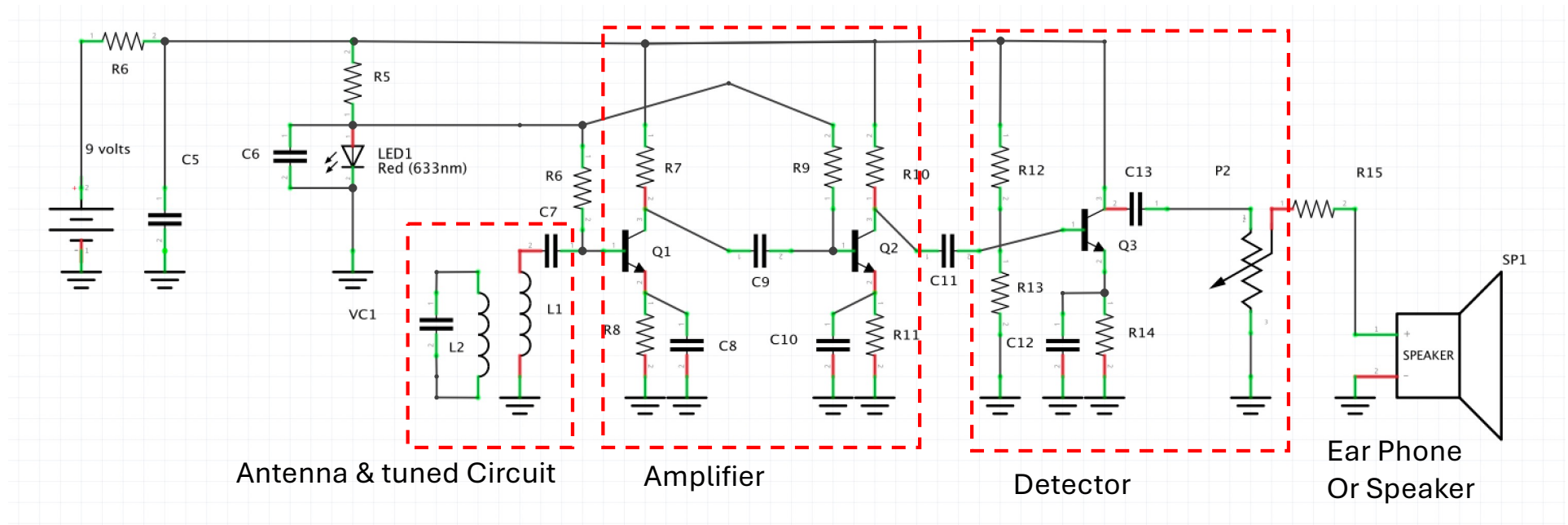

# Regenerative Receiver

- The original patent for the regenerative receiver was filed by Edwin Armstrong in 1914
- He demonstrated it at the Marconi site (across the road from CDL)
- It uses an RF amplifier that feeds some of the output back into the input
- The amount of feedback is adjusted by a regeneration control and is adjust to make the amplifier gain be just before it starts oscillating
- A regenerative receiver can be made very sensitive to receiver very weak signals
- The regeneration stage typically also detects the AM signal
- Putting it into oscillation can make it receiver CW signals

# Block Diagram of Regenerative Receiver

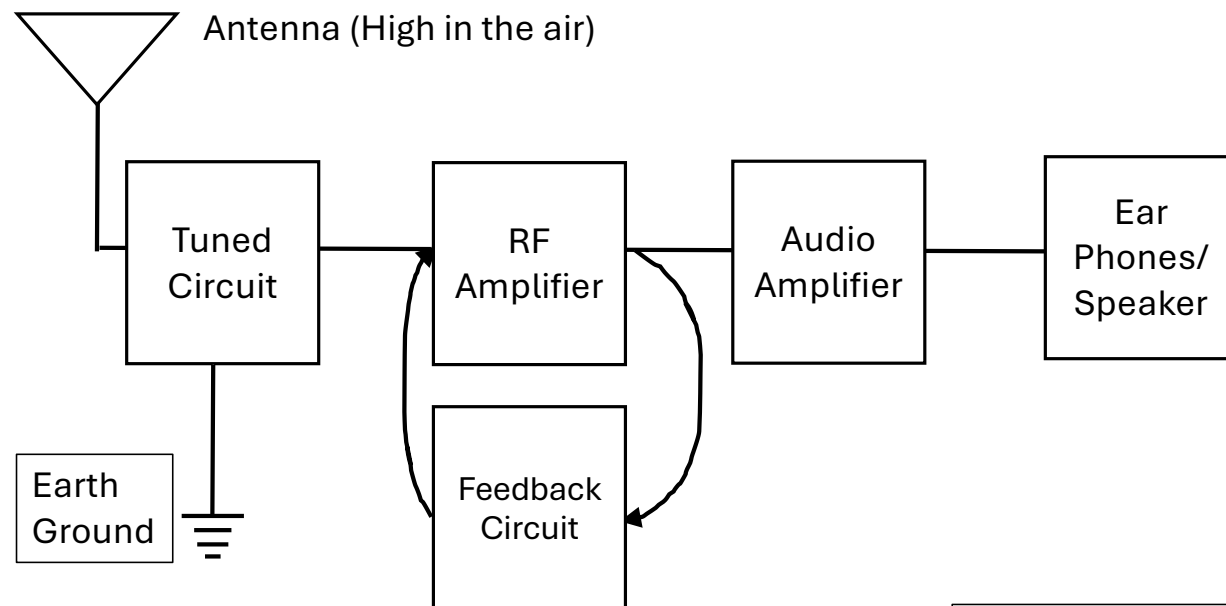


# Example Regenerative Receiver with Tubes

8/17/04
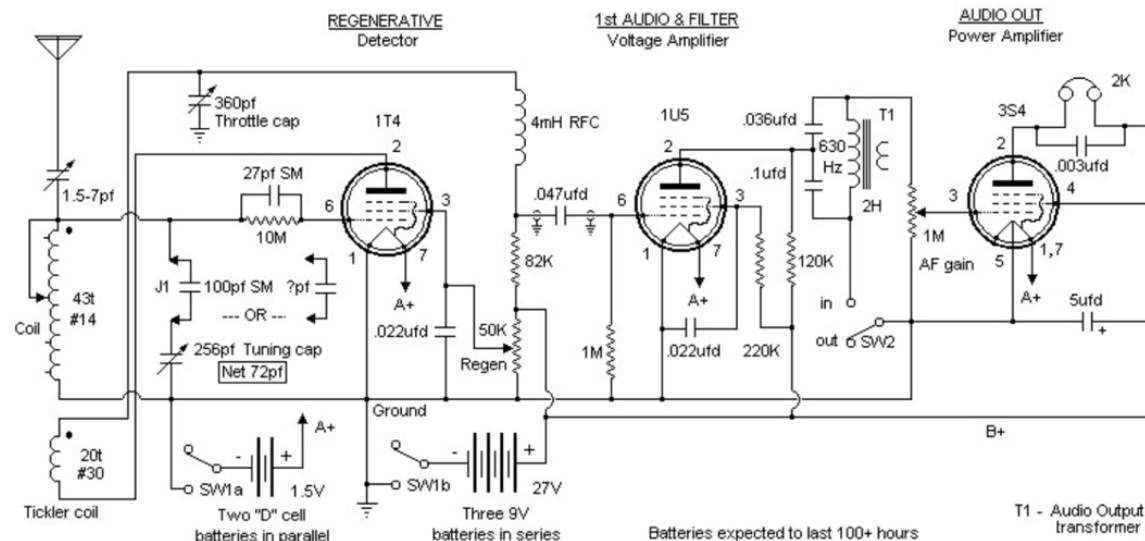
## K5BCQ BATTERY POWERED REGENERATIVE TUBE RECEIVER

170ma at 1.5VDC and 6ma at 27VDC  
w/ ZL2JJ Audio Filter



Coil taps (not critical):  
35.2uH J1 = jumper 1.5Mhz - 4.0 Mhz  
12.4uH  
5.6uH  
1.3uH

Homebrew:  
Nothing is critical, use what you have and try it

Coil notes:  
Ceramic coil form 2" dia and 5" long (surplus)  
Molex connector tap selection  
Tickler coil spaced 1/8" away on ground end

Build notes:  
Short leads, heavy gauge wire, careful RF layout  
Tuning mechanism from a BC-221 (excellent drive)  
Ceramic Regen tube socket w/shield  
Use Mylar caps in the audio section Poly is OK  
Don't use ceramic  
Use Silver Micas where indicated  
Grids referenced to pin 1 and 5




## Example Regenerative Receiver with Transistors and Integrated circuits

**For more information:**

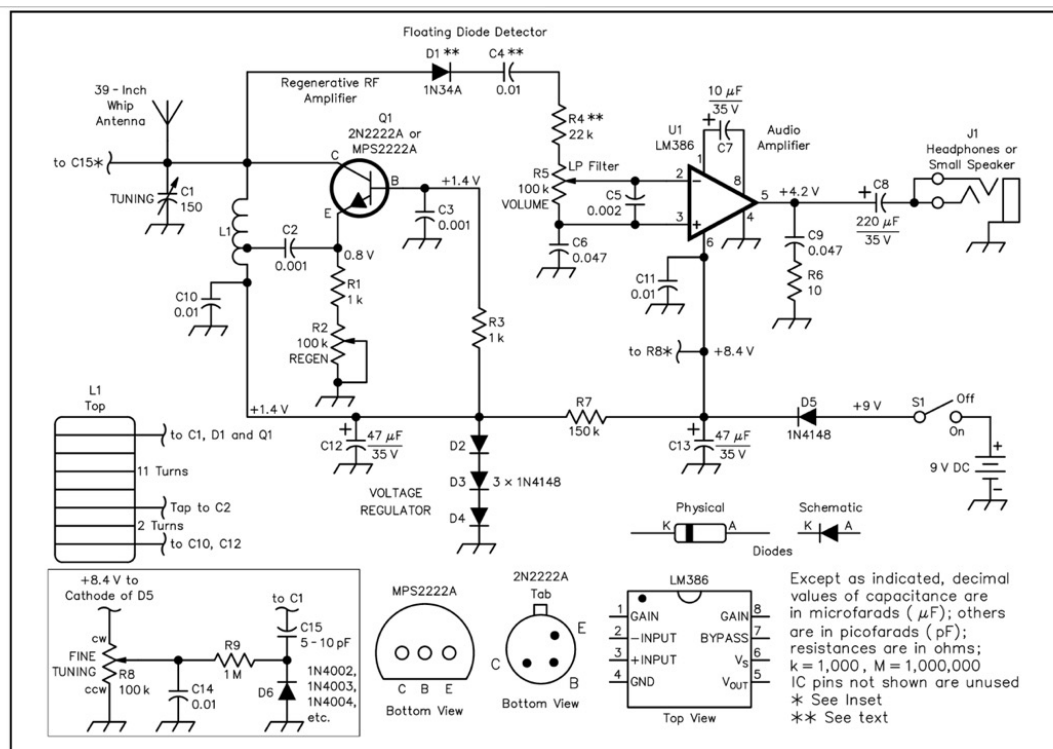**Click on the link and read article**

<https://www.arrl.org/files/file/Technology/tis/info/pdf/0009061.pdf>



## Simple Regen Receiver From QST

# Super-Regenerative Receiver

- In a Super Regenerative Receiver, the circuit is made to in and out of oscillation at a rate around 50,000-100,000 times per second
- Thus, no regeneration control is needed
- The receiver is very sensitive
- However, nearby (in frequency or location) transmitters can overload the receiver and prevent receiving the desired signal

# Example Super-Regenerative Receiver

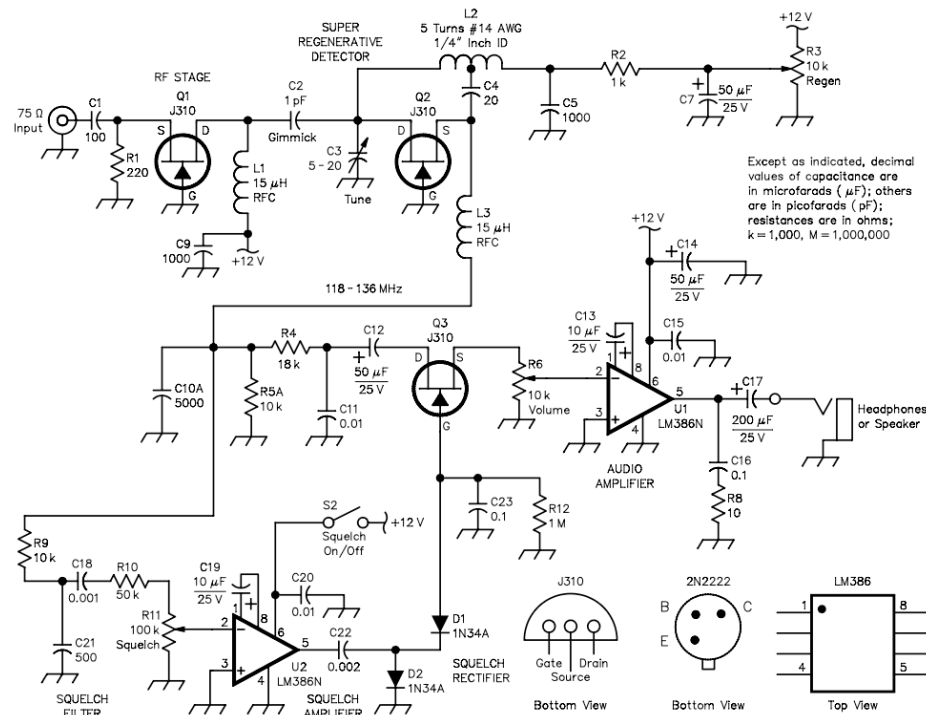


Fig 12—A super-regen VHF aircraft-band (118-136 MHz) receiver with squelch.

QEX- Sept/Oct 2000 27

For more information click on link and read the article  
[new\\_super\\_regen\\_for\\_vhf\\_uhf\\_2000\\_09qex018.pdf](#)

January 2026


# Disadvantages of Regenerative Receiver

- It takes skill to adjust the receiver
- The control needs to be adjusted often from:
  - The antenna swaying in the wind
  - Changes in frequency of the receiver
- When a super regenerative or regenerative receiver goes into oscillation it radiates a signal like a transmitter
  - This can interfere with other receivers nearby
  - The Nazi's used this to direction find underground stations when the operators mis-adjusted their receivers and left them on


# Superheterodyne Receiver

- Lucien Lévy: Patented the fundamental circuit scheme for the superheterodyne receiver in 1917
- Edwin H. Armstrong: Developed a more practical version of the superheterodyne method and was granted U.S. patent 1,342,885 in 1920 for his work
- In a Superheterodyne receiver, the received frequency is changed to a (typically) lower frequency where:
  - Gain and
  - Selectivity is easier to design into the circuits
- But, unless superhet receivers are correctly designed, they can pick interference from other frequencies than the desired frequency

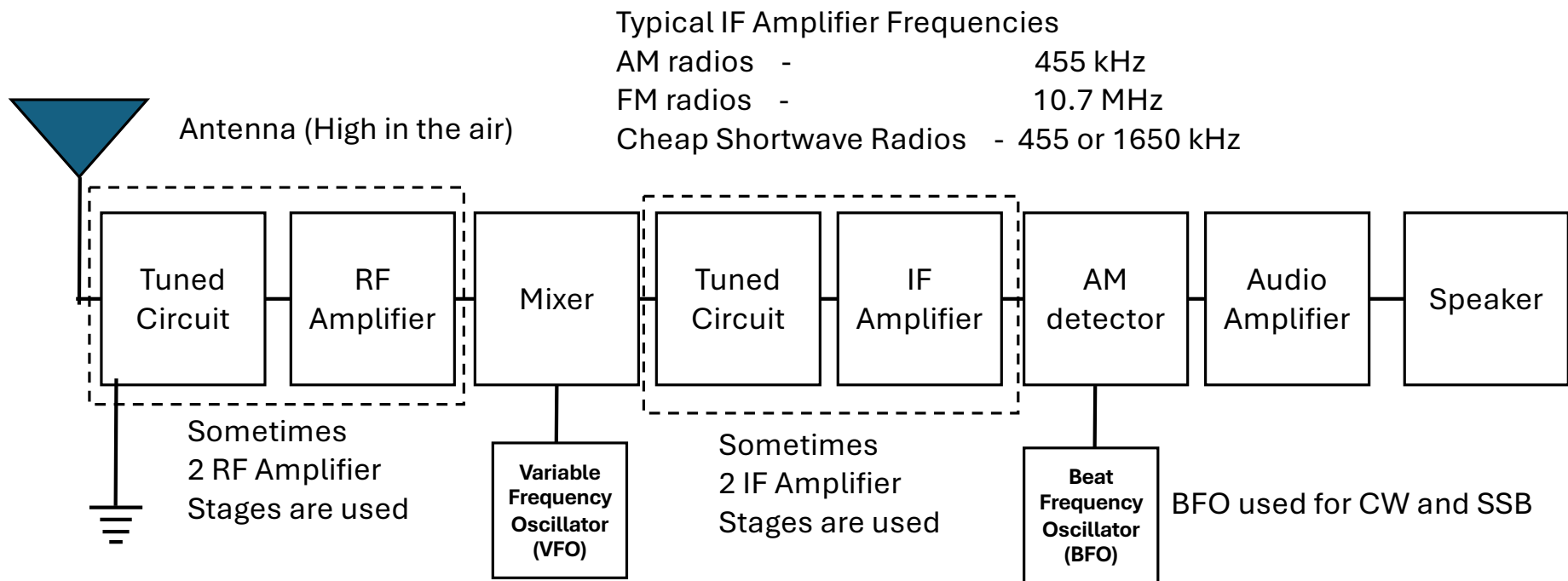
# Block Diagram of Superheterodyne Receiver


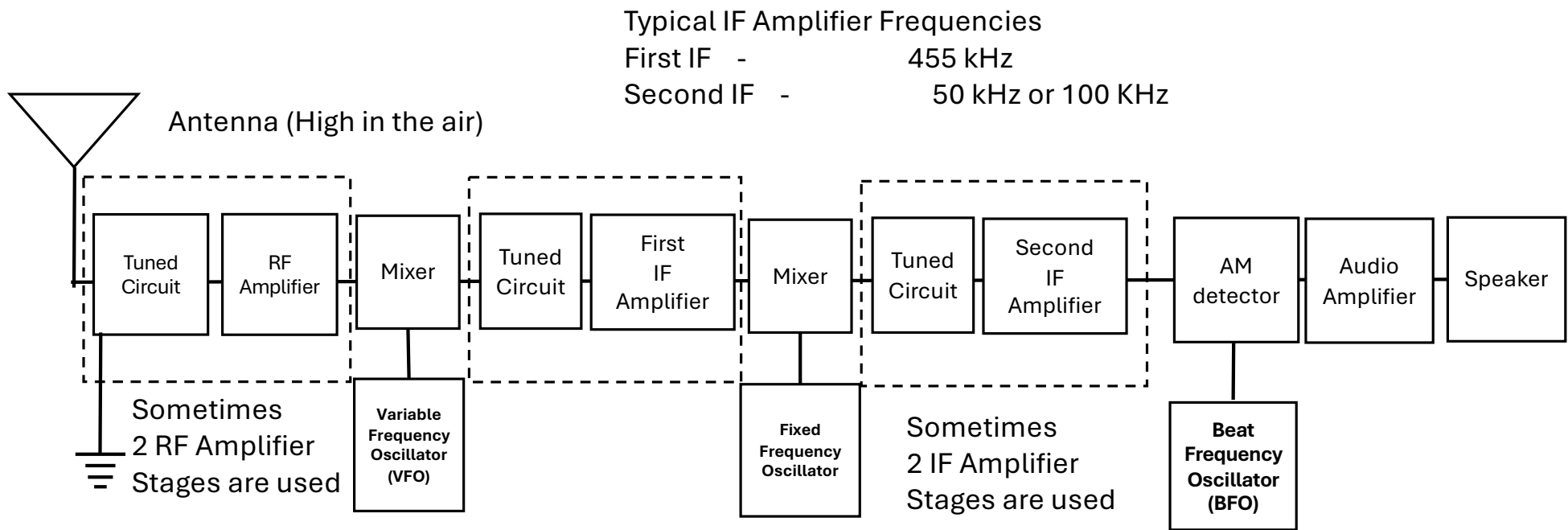
# Block Diagram of Double Conversion Superheterodyne Receiver


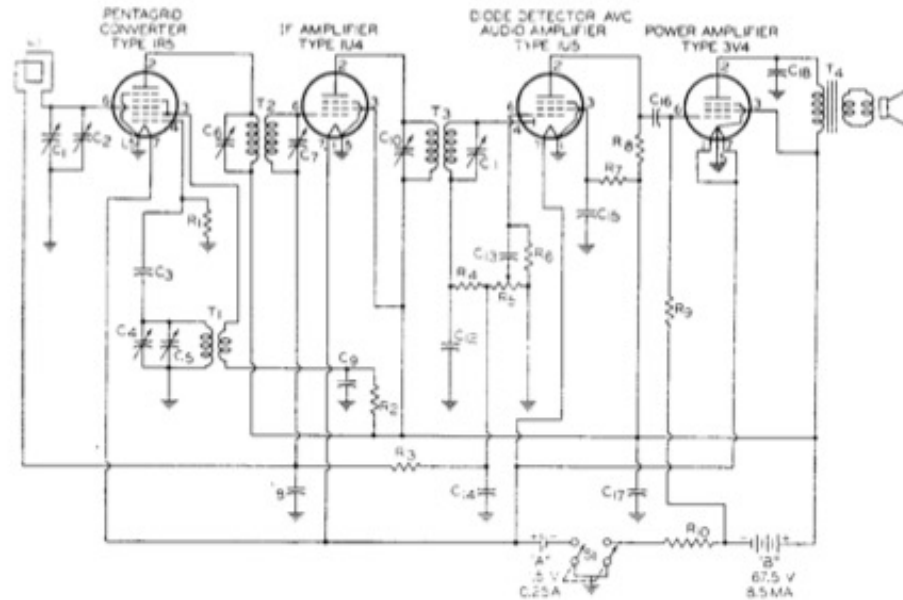
## PORTABLE BATTERY-OPERATED SUPERHETERODYNE RECEIVER



C<sub>1</sub>, C<sub>4</sub> = Ganged tuning capacitors: C<sub>1</sub>, 10-274  $\mu$ f; C<sub>4</sub>, 7.5-122.5  $\mu$ f  
 C<sub>2</sub>, C<sub>5</sub> = Trimmer capacitors, 2-15  $\mu$ f  
 C<sub>3</sub> = 56  $\mu$ f, ceramic  
 C<sub>6</sub>, C<sub>7</sub>, C<sub>10</sub>, C<sub>11</sub> = Trimmer capacitors for if transformers  
 C<sub>8</sub> = 0.05  $\mu$ f, paper, 50 v.  
 C<sub>9</sub>, C<sub>12</sub> = 0.02  $\mu$ f, paper, 100 v.  
 C<sub>13</sub> = 82  $\mu$ f, ceramic  
 C<sub>14</sub>, C<sub>15</sub> = 0.002  $\mu$ f, paper, 150 v.  
 C<sub>16</sub> = 33  $\mu$ f, ceramic

C<sub>17</sub> = 10  $\mu$ f, electrolytic, 100 v.  
 C<sub>18</sub> = 0.0022  $\mu$ f, paper, 600 v.  
 L<sub>1</sub> = Loop antenna, 540-1600 Kc  
 R<sub>1</sub> = 100000 ohms, 0.25 watt  
 R<sub>2</sub> = 15000 ohms, 0.25 watt  
 R<sub>3</sub> = 3.3 megohms, 0.25 watt  
 R<sub>4</sub> = 68000 ohms, 0.25 watt  
 R<sub>5</sub> = Volume control, potentiometer, 2 megohms  
 R<sub>6</sub> = 10 megohms, 0.25 watt  
 R<sub>7</sub> = 4.7 megohms, 0.25 watt  
 R<sub>8</sub>, R<sub>9</sub> = 1 megohm, 0.25 watt

R<sub>10</sub> = 390 ohms, 0.25 watt  
 S<sub>1</sub> = Switch, double-pole, single-throw  
 T<sub>1</sub> = Oscillator coil for use with tuning capacitor of 7.5-122.5  $\mu$ f, and 455 Kc if transformer  
 T<sub>2</sub>, T<sub>3</sub> = Intermediate-frequency transformers, 455 Kc  
 T<sub>4</sub> = Output transformer for matching impedance of voice coil to 10000-ohm tube load

# Superhet Receiver from RCA Receiving Tube Manual


January 2026

For free RCA manuals see <https://www.worldradiohistory.com/BOOKSHELF-ARH/Technology/RCA-Books/>  
 And click on the link for the receiving tube manual you want to read  
 for example RCA-Receiving-Tube-Manual-1960-RC-20.pdf




# Demodulation of AM

- The simplest way to detect AM is to rectify the received signal
- Then filter out the RF leaving just the audio signal

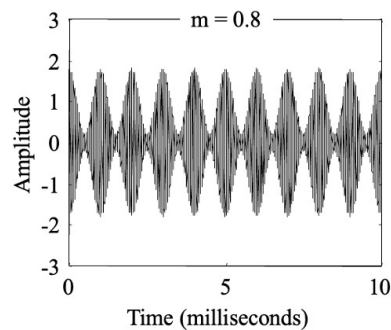


January 2026

Diode  
Rectifier

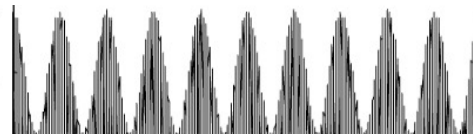


RF Filter

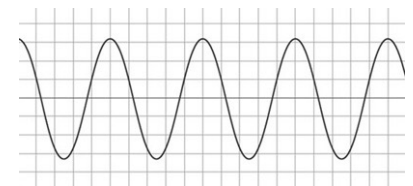
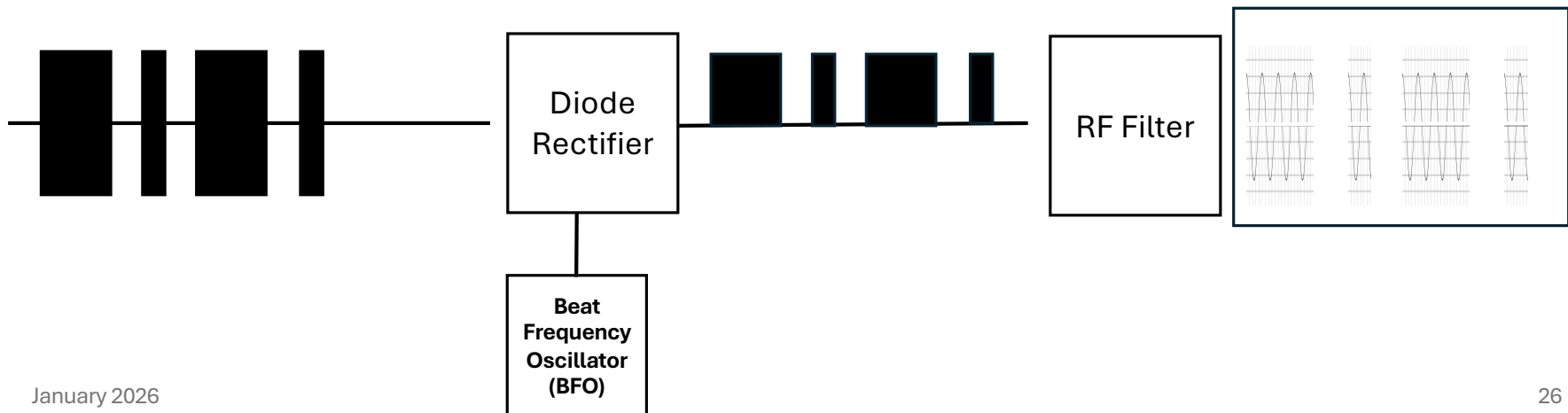
# Demodulation of CW

- The simplest way to demodulate CD is to use an AM detector and add an RF or IF signal 400 Hz to 1.5 kHz from the received signal
- The detector mixes the two signals together and generates a tone when the CW signal is present




# Demodulation of Single Side Band (SSB)

- Demodulation of SSB is similar to that of CW
- But the BFO signal needs to be within less than 100 Hz of the missing carrier signal
- Early SSB receivers tended to drift off frequency and the received signal had distortion that made its sound like “Donald Duck”
- This limited adoption of SSB in the 50s and 60s
- Modern SSB receivers use a mixer instead of an AM detector
- They also can be tuned and stay tuned to within a few Hz of the mixing carrier
- Some receivers have GPS built-in or accept timing information from a GPS receiver to make the tuning very precise (less than 1 Hz of error)
- The speech sounds natural

# Demodulation of FM and PM


- Demodulation of FM in a receiver needs to additional circuits compared to an AM receiver
- An IF amplifier that limits the maximum signal and thus clips it to a constant level
- An FM detector that uses a special coil called a discriminator coil and two diodes

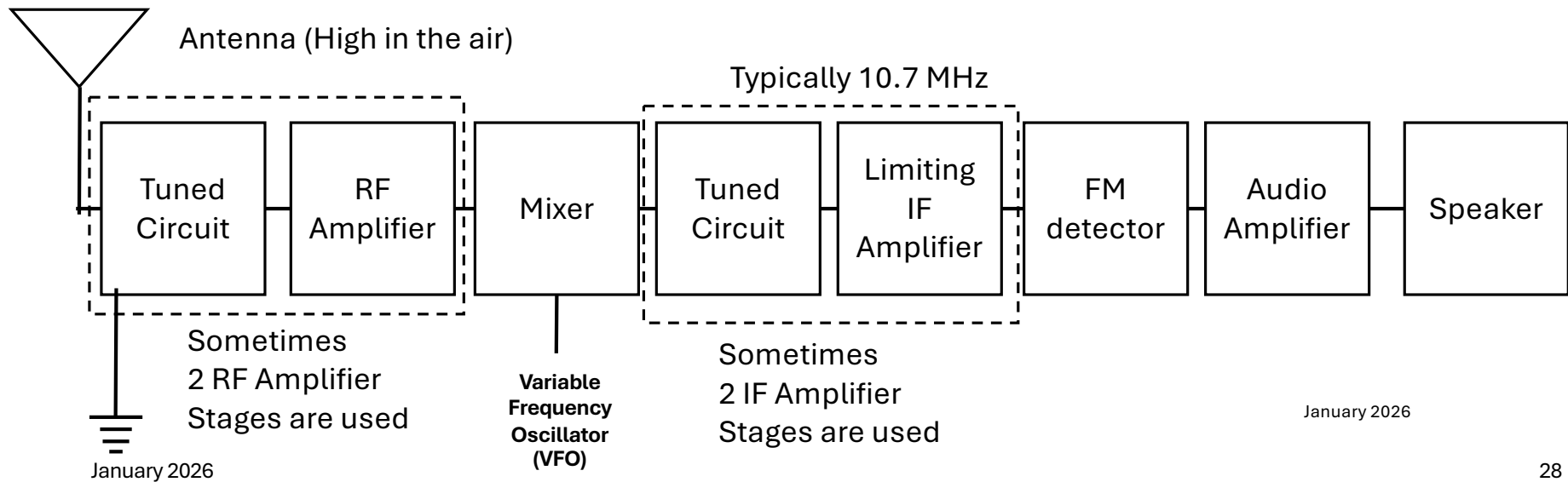

January 2026
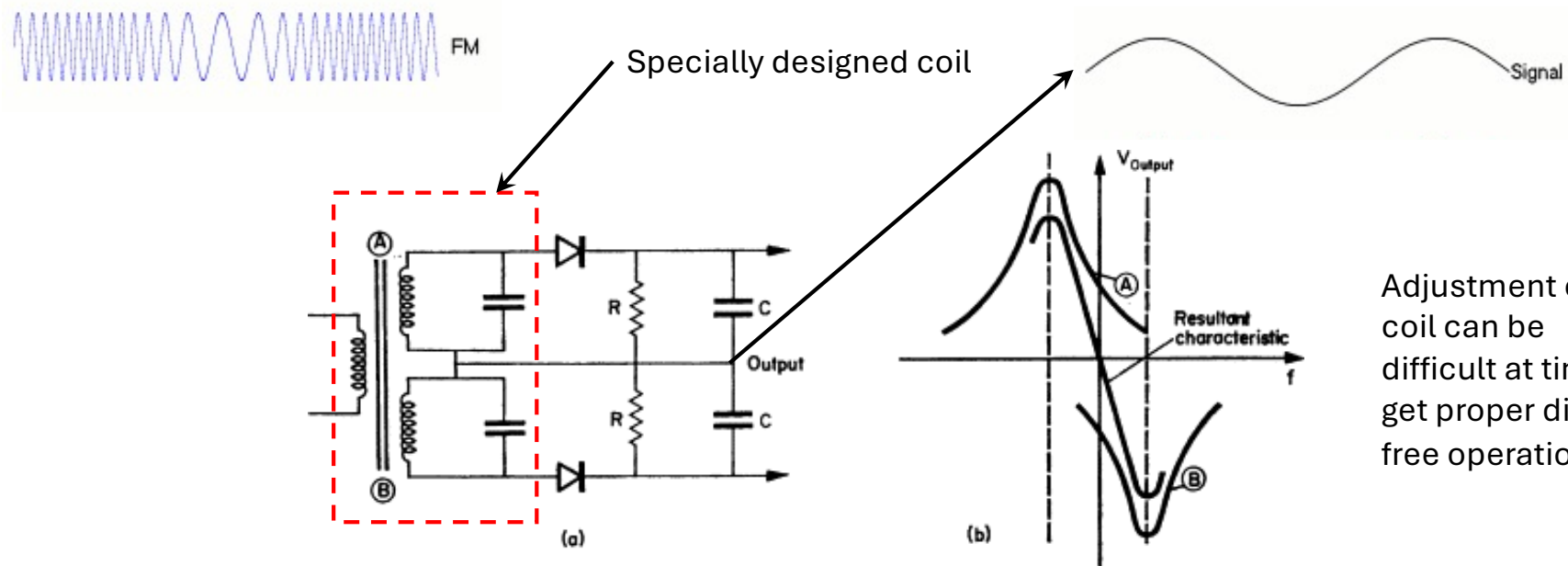
# Discriminator Operation

The output changes with the changes in frequency



# References

- Recommended Textbooks
- ARRL: *The ARRL Handbook for Radio Communications*
- Make: *Radio*
- *Old but still good reference:*
- Rappaport, *Wireless Communications: Principles and Practice*
- Goldsmith, *Wireless Communications*
- Molisch, *Wireless Communications*
- Garg and Wilkes, *Wireless and Personal Communications Systems*
- Useful Online Resources
- FCC Spectrum Allocation Charts
- 3GPP Specifications (for LTE/5G)
- IEEE 802.11 Standards overview
- ITU Radio Regulations
- Simulation Tools
- MATLAB/Simulink Wireless Toolbox
- Python libraries: scipy, matplotlib, commpy
- Free online spectrum analyzers & demos